

FUNDAMENTALS OF POWER ELECTRONICS

Dinesh Gopinath
dinesh@cet.ac.in

Department of Electrical Engineering
College of Engineering, Trivandrum



- Power Electronics: Goals and Functions
- Switches: Ideal to Practical

- **Efficient Conversion, Conditioning and Control** of Electrical Energy using Power Semiconductor Devices and Passive elements.
 - Use of Semiconductor Devices as 'Switches'
 - Switching Vs Linear Power Electronics
 - Say 'NO' to R, 'YES' to L and C!!
 - Circuits: AC-DC, DC-DC, DC-AC and AC-AC
 - Reactive Elements: L, C \rightarrow energy storage, filters and snubbers
 - Control methods to 'shape' voltages and currents
 - Digital/Analog Control: Algorithms and methods

- **Efficient Conversion, Conditioning and Control** of Electrical Energy using Power Semiconductor Devices and Passive elements.
 - Use of Semiconductor Devices as 'Switches'
 - Switching Vs Linear Power Electronics
 - Say 'NO' to R, 'YES' to L and C!!
 - Circuits: AC-DC, DC-DC, DC-AC and AC-AC
 - Reactive Elements: L, C \rightarrow energy storage, filters and snubbers
 - Control methods to 'shape' voltages and currents
 - Digital/Analog Control: Algorithms and methods

- **Efficient Conversion, Conditioning and Control** of Electrical Energy using Power Semiconductor Devices and Passive elements.
 - Use of Semiconductor Devices as 'Switches'
 - Switching Vs Linear Power Electronics
 - Say 'NO' to R, 'YES' to L and C!!
 - **Circuits: AC-DC, DC-DC, DC-AC and AC-AC**
 - Reactive Elements: L, C \rightarrow energy storage, filters and snubbers
 - Control methods to 'shape' voltages and currents
 - Digital/Analog Control: Algorithms and methods

- **Efficient Conversion, Conditioning and Control** of Electrical Energy using Power Semiconductor Devices and Passive elements.
 - Use of Semiconductor Devices as 'Switches'
 - Switching Vs Linear Power Electronics
 - Say 'NO' to R, 'YES' to L and C!!
 - Circuits: AC-DC, DC-DC, DC-AC and AC-AC
 - **Reactive Elements: L, C** → energy storage, filters and snubbers
 - **Control methods to 'shape' voltages and currents**
 - Digital/Analog Control: Algorithms and methods

- **Efficient Conversion, Conditioning and Control** of Electrical Energy using Power Semiconductor Devices and Passive elements.
 - Use of Semiconductor Devices as 'Switches'
 - Switching Vs Linear Power Electronics
 - Say 'NO' to R, 'YES' to L and C!!
 - Circuits: AC-DC, DC-DC, DC-AC and AC-AC
 - **Reactive Elements: L, C** —> energy storage, filters and snubbers
 - **Control methods** to 'shape' voltages and currents
 - **Digital/Analog Control: Algorithms and methods**

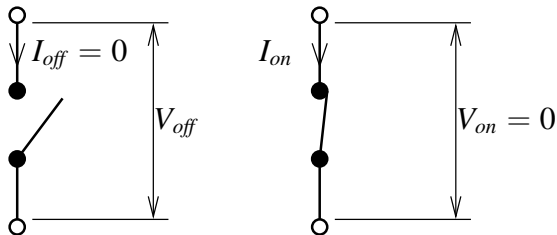


FIGURE: Ideal Switch

- Infinite I_{on} and V_{off}
- Zero I_{off} and V_{on}
- Zero t_{on} and t_{off}
- Zero Temperature rise
- Zero energy to turn ON/OFF and maintain states
- Infinite "Power-to-Weight" or "Power-to-Volume" ratio
- Zero Cost!!!

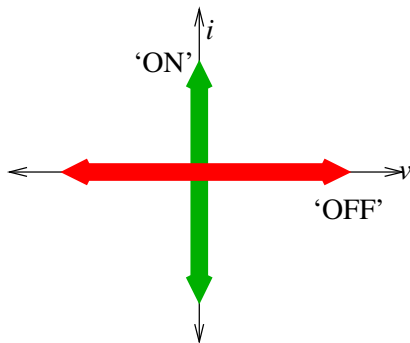


FIGURE: Ideal Switch Characteristics

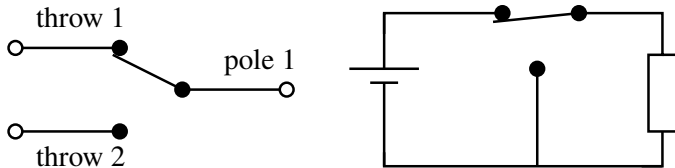


FIGURE: Ideal SPDT Switch and its use in Buck converter

- Two states

Ideal Switches : SPDT and SPTT

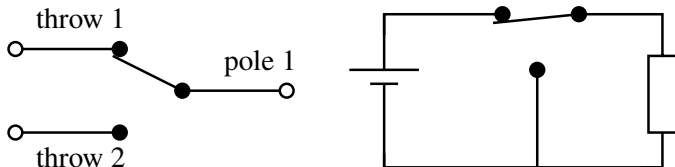


FIGURE: Ideal SPDT Switch and its use in Buck converter

- Two states

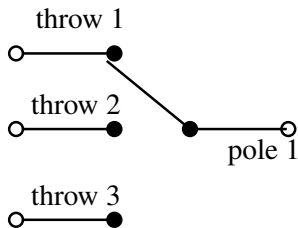


FIGURE: Ideal Single Pole Triple Throw Switch

The Realities: Switches Do not 'Know' KVL and KCL!

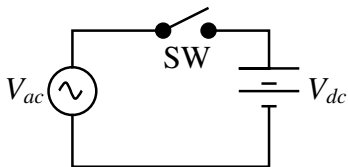


FIGURE: KVL: Switch SW must always be 'OFF'

- Dangerous to switch between two “Voltage-stiff” circuits!!
- KVL causes large currents to flow
- FIRE! in practical cases

The Realities: Switches Do not 'Know' KVL and KCL!

- Dangerous to switch between two “Current-stiff” circuits!!
- KCL causes large voltages to be induced
- Damages due to high-voltages in practical cases

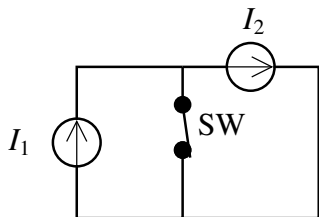


FIGURE: KCL: Switch SW must always be 'ON'

The Realities: Switches Do not 'Know' KVL and KCL!


- Switchings can be done **ONLY** between a **Voltage-stiff** circuit and a **Current-stiff** circuit
- Long-term KVL problem : Voltage switched in to an Inductor
- Long-term KCL problem : Current switched in to a Capacitor

- The Non-idealities

- V_{off} and I_{on} are finite, limited values : Limited blocking voltage, limited current capacity
- V_{on} and I_{off} are non-zero values : ON-state and OFF-state losses
- t_{on} , t_{off} are non-zero values : Non-zero switching losses
- Non-zero drive energy : Losses in drive circuits
- Power and thermal limits : Power and Temperature limits
- Safe Operating Area


- The Non-idealities

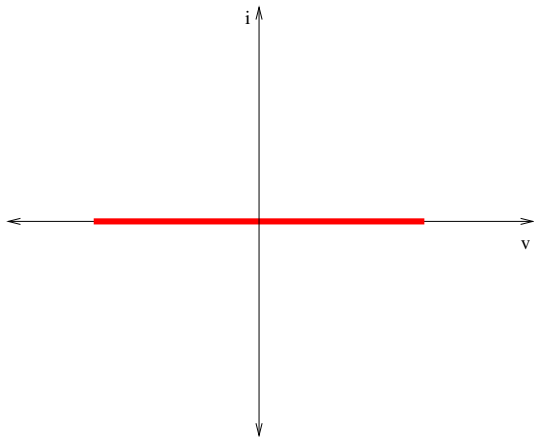- V_{off} and I_{on} are finite, limited values : **Limited blocking voltage, limited current capacity**
- V_{on} and I_{off} are non-zero values : **ON-state and OFF-state losses**
- t_{on} , t_{off} are non-zero values : **Non-zero switching losses**
- Non-zero drive energy : **Losses in drive circuits**
- Power and thermal limits : **Power and Temperature limits**
- **Safe Operating Area**




- The Non-idealities

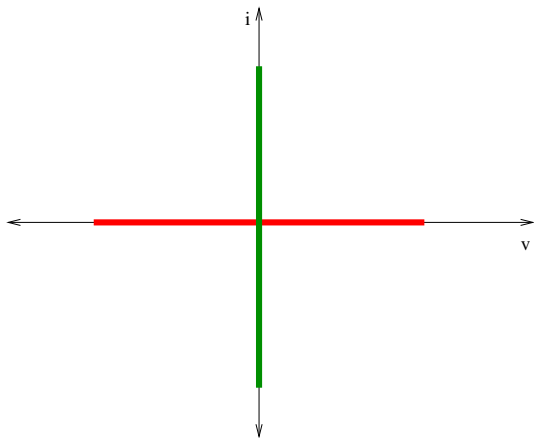- V_{off} and I_{on} are finite, limited values : **Limited blocking voltage, limited current capacity**
- V_{on} and I_{off} are non-zero values : **ON-state and OFF-state losses**
- t_{on} , t_{off} are non-zero values : **Non-zero switching losses**
- Non-zero drive energy : **Losses in drive circuits**
- Power and thermal limits : **Power and Temperature limits**
- **Safe Operating Area**




- The Non-idealities

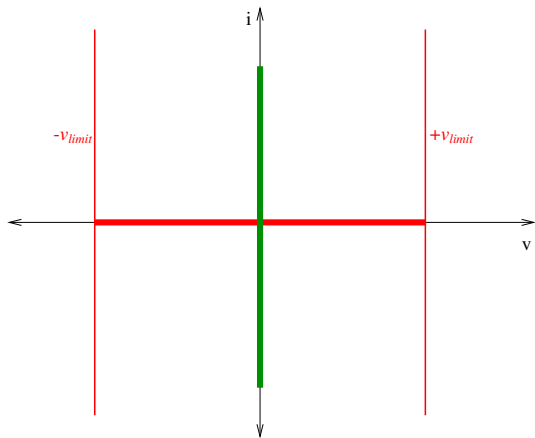- V_{off} and I_{on} are finite, limited values : **Limited blocking voltage, limited current capacity**
- V_{on} and I_{off} are non-zero values : **ON-state and OFF-state losses**
- t_{on} , t_{off} are non-zero values : **Non-zero switching losses**
- Non-zero drive energy : **Losses in drive circuits**
- Power and thermal limits : **Power and Temperature limits**
- **Safe Operating Area**




- The Non-idealities

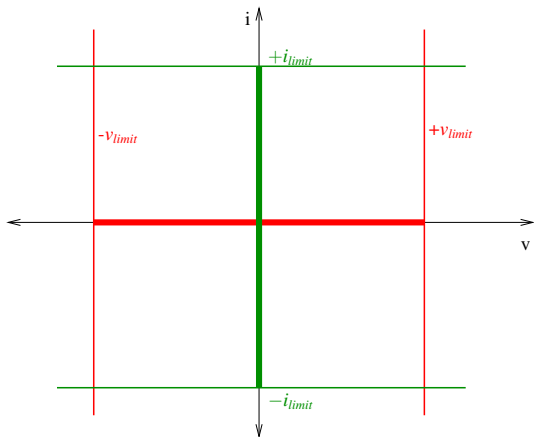- V_{off} and I_{on} are finite, limited values : Limited blocking voltage, limited current capacity
- V_{on} and I_{off} are non-zero values : ON-state and OFF-state losses
- t_{on} , t_{off} are non-zero values : Non-zero switching losses
- Non-zero drive energy : Losses in drive circuits
- Power and thermal limits : Power and Temperature limits
- Safe Operating Area




- The Non-idealities

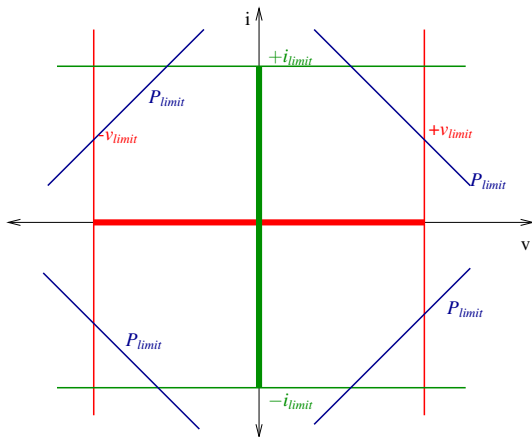- V_{off} and I_{on} are finite, limited values : Limited blocking voltage, limited current capacity
- V_{on} and I_{off} are non-zero values : ON-state and OFF-state losses
- t_{on} , t_{off} are non-zero values : Non-zero switching losses
- Non-zero drive energy : Losses in drive circuits
- Power and thermal limits : Power and Temperature limits
- Safe Operating Area




- The Non-idealities

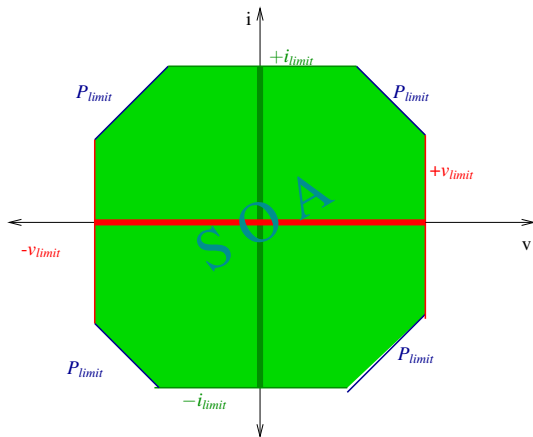- V_{off} and I_{on} are finite, limited values : Limited blocking voltage, limited current capacity
- V_{on} and I_{off} are non-zero values : ON-state and OFF-state losses
- t_{on} , t_{off} are non-zero values : Non-zero switching losses
- Non-zero drive energy : Losses in drive circuits
- Power and thermal limits : Power and Temperature limits
- Safe Operating Area



- Three States
 - Static States: ON and OFF
 - Dynamic State: Commutation or Transition
 - Energy losses in ALL THREE states

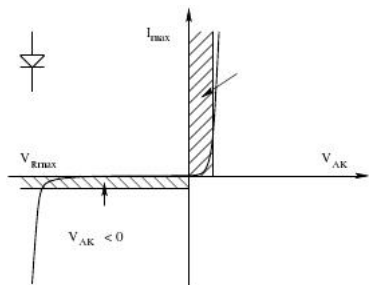- Current Ratings in ON state
 - Continuous current : Worst case design
 - Average Current : ON-state loss
 - RMS current : ON-state Losses
 - Peak current : Local heating and metal contacts
 - Current-time values : Peak current for short duration: Duty Cycle



- PN, PiN, Schottky
- 1A to 5000A+
- 10V to 10kV+
- 20 ns to 100 μ s
- Data sheet

FIGURE: Diode Characteristics

- Operating Quadrants: Forward Conduction, Reverse Blocking
- Non-idealities: r_d , V_f , I_{off} , V_{PIV}
- Static and Dynamic performance
 - Reverse Recovery: *Snap* and *Soft* :(Diffusion Capacitance)
- Important Specs:
 - I_F , V_{PIV} , V_F , I_{off} , Z_{th} , t_{rr} , I^2T
- Static Equivalent Circuit

Practical Semi-Controlled Switches: SCR and Triac

- Charge/Current Controlled
- Operating Quadrants: Forward Conducting, Forward and Reverse Blocking
- External Turn-off control not possible
- 1A-5000A
- 200V-6000V
- $1\mu s$ - $200\mu s$
- Two-Transistor equivalent circuit:
- Important Specs: I_F , V_{RRM} , V_F , I_{off} , $\frac{di}{dt}$, $\frac{dv}{dt}$, Z_{th} , t_q , I^2t
- Static and Dynamic Characteristics
- Turn ON and Turn OFF conditions
- Data Sheet
- Triac : 2A-50A, 200V-800V


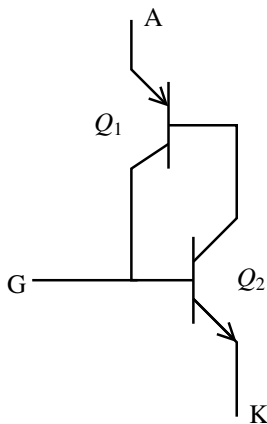


FIGURE: Two-Transistor model:



$$I_A = \frac{\alpha_2 I_g + I_{cbo1} + I_{cbo2}}{1 - (\alpha_1 + \alpha_2)}$$

- Base region is wider than small-signal BJT
- Current Controlled
- Low Current Gain: **Increased drive power requirement, losses, slow switching**
- 0.5A-500A+
- 30V-1200V
- $0.5\mu s$ - $100\mu s$
- Operating Quadrants: Forward Conducting, Forward Blocking
- Data Sheet


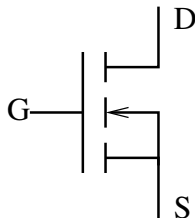
- Voltage controlled: **Low drive power requirements, fast switching**
- Operating Quadrants: Forward/Reverse Conducting, Forward Blocking (Body Diode)
- 1A-100A+
- 30V-1000V
- 50 ns - 200 ns
- Important Specs: I_D , I_M , BV_{DSS} , $r_{ds(on)}$, Z_{th} , t_{on} , t_{off} , V_{gs} , R_{gs} , $V_{gs(th)}$, I_{SD} , t_{rr} , C_{iss}
- Data Sheet




Practical Controlled Switches: MOSFETs

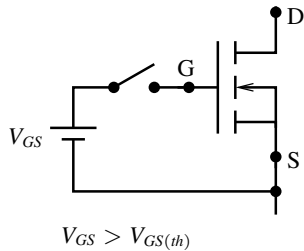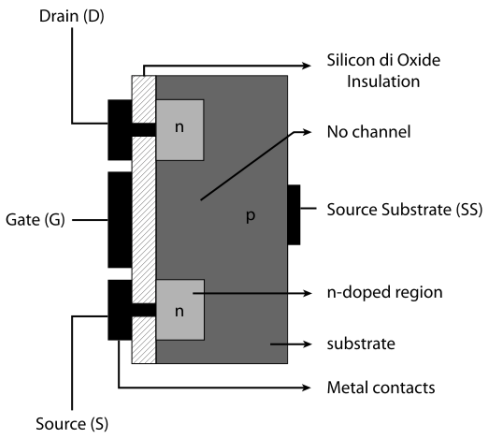


Practical Controlled Switches: MOSFETs

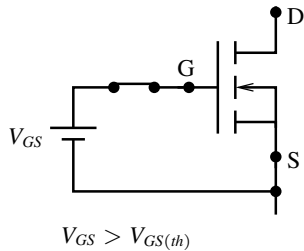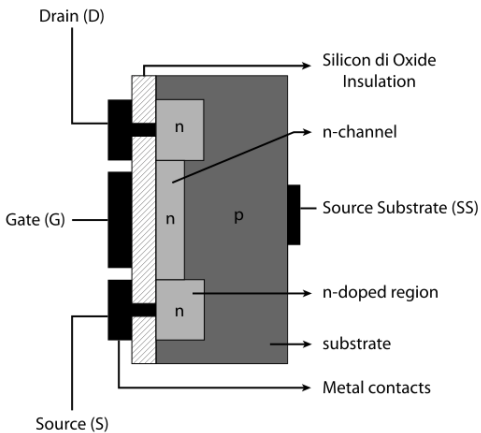

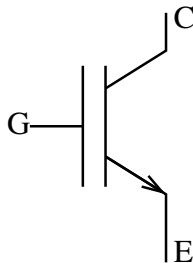
- Voltage Controlled: Like MOSFET
- Faster than BJTs, slower than MOSFETs
- Operating Quadrants: Forward Conducting, Forward Blocking
- 10A-1200A+
- 600V-3300V
- 500 ns -
- Important Specs: I_D , I_M , BV_{DSS} , $r_{ds(on)}$, Z_{th} , t_{on} , t_{off} , V_{gs} , R_{gs} , $V_{gs(th)}$, I_{SD} , t_{rr} , C_{iss}
- Data Sheet




Equivalent Circuit

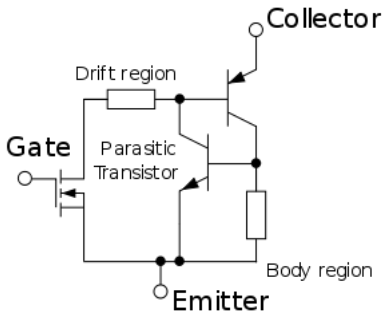


Structure of IGBT

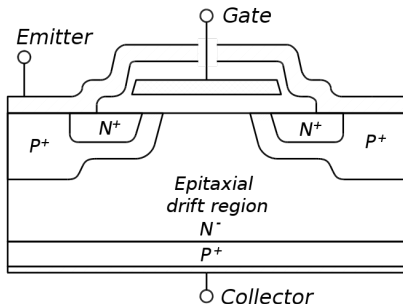


Equivalent Circuit

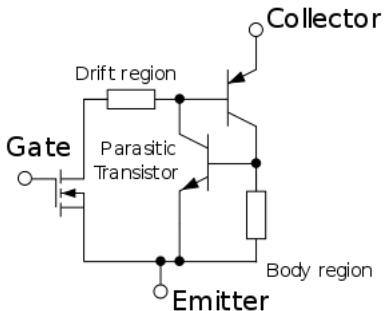

Structure of IGBT

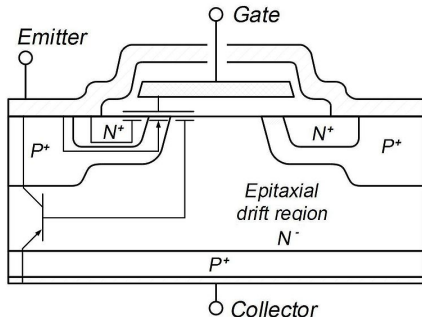

Practical Controlled Switches: IGBTs

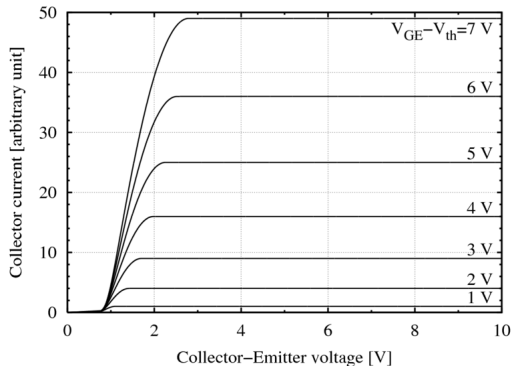

Gate Drive Circuits