

# Power Electronics



---

## TRIGGERING CIRCUITS

2018


*Dr. Francis M. Fernandez*

# Gate Characteristics

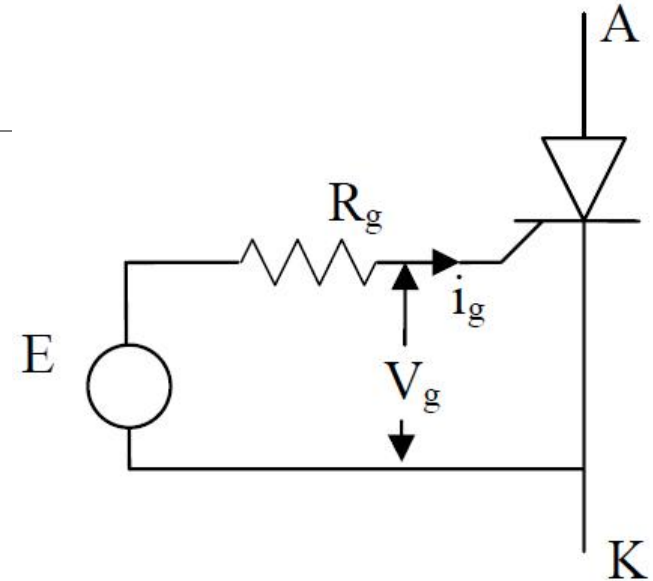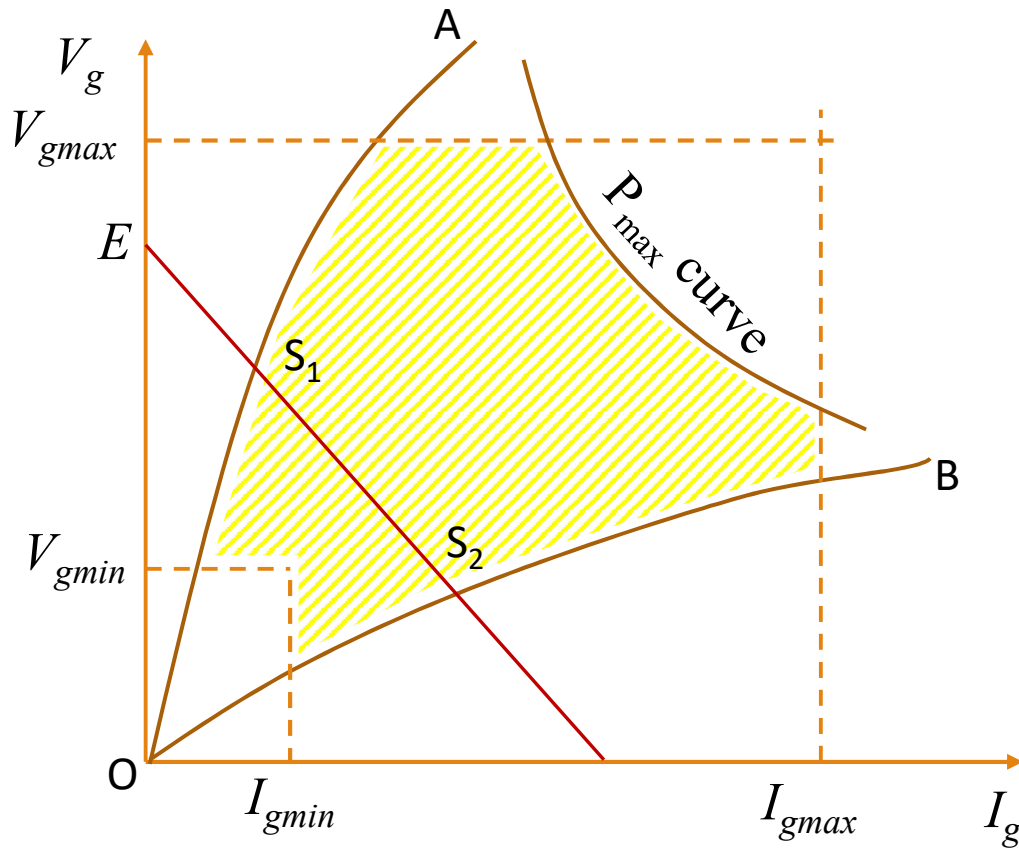

OA and OB represent the spread of characteristics for the thyristor of same rating

# R - Triggering Circuit

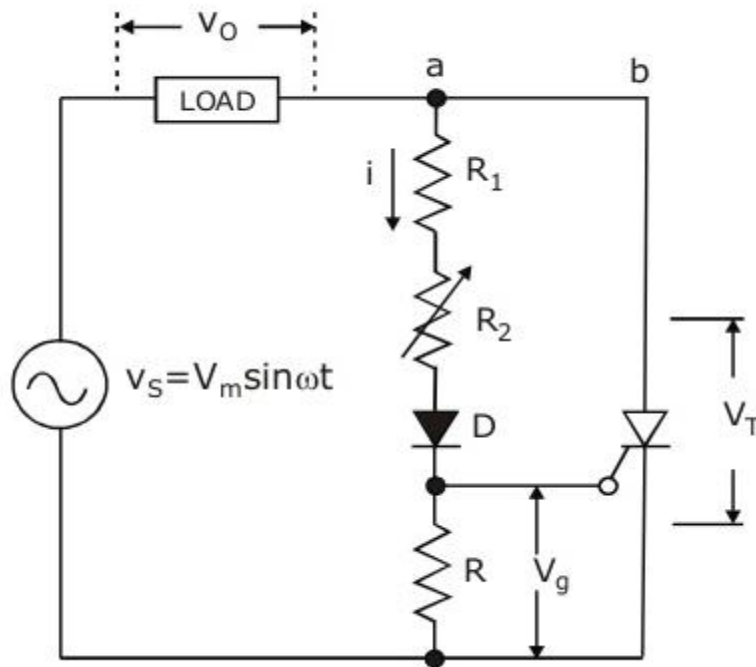

- $R_1$  is the gate current limiting resistance
- $R_2$  is used to vary the gate current and hence firing angle



$$I_{g \max} = \frac{V_m}{R_1} \quad \Rightarrow \quad R_1 \geq \frac{V_m}{I_{g \max}}$$

- $R$  limits the voltage at Gate terminal

$$R \leq \frac{V_{g \max} R_1}{V_m - V_{g \max}}$$

- Diode D prevents build-up of negative voltage at Gate terminal



# R-Trig Waveforms

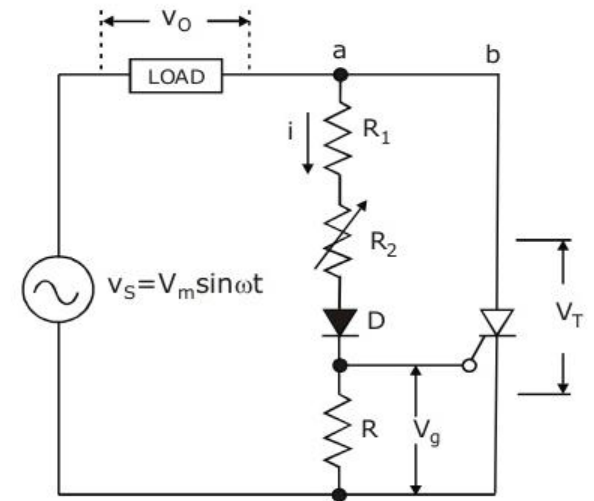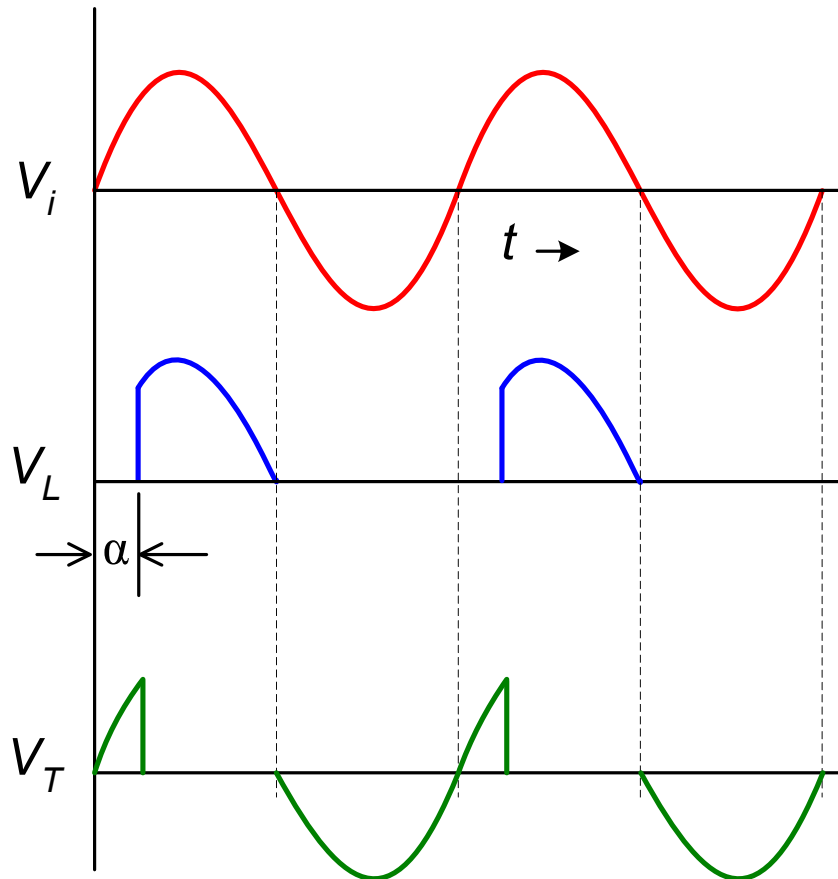

- The phase angle at which the SCR starts conducting is called **firing angle,  $\alpha$**
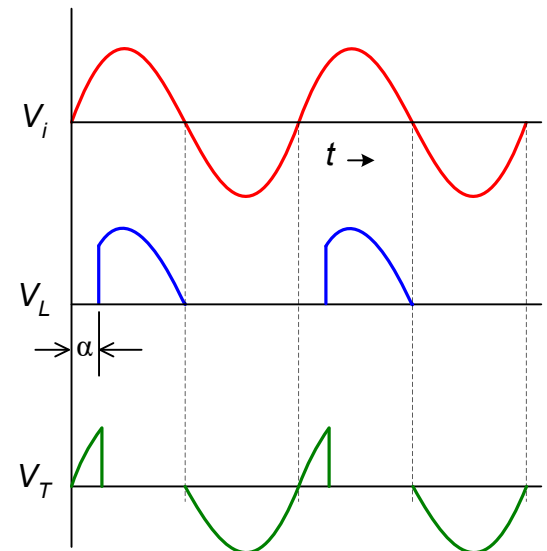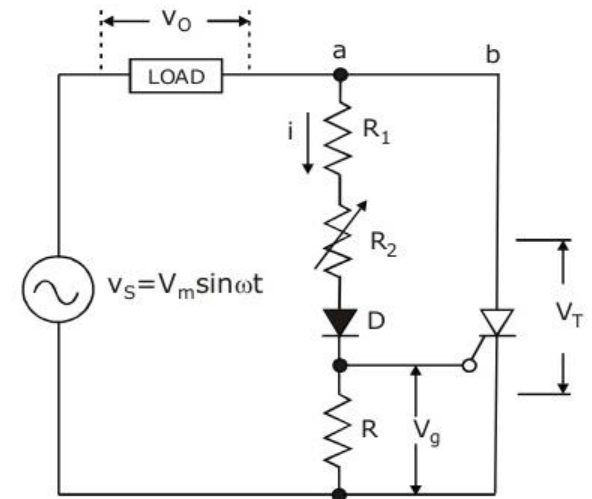
# Features of R-Trig Circuit

- ❑ Simple circuit
- ❑ Disadvantages:
  - Performance depends on temperature and SCR characteristics
  - Minimum phase angle is typically 2-4 degrees only (not zero degree)
  - Maximum phase angle is only 90 degrees



# Problem

Design an R-triggering circuit for a half wave controlled rectifier circuit for 24 V ac supply. The SCR to be used has the following data.

$$I_{gmin} = 0.1 \text{ mA}, \quad I_{gmax} = 12 \text{ mA}, \quad V_{gmin} = 0.6\text{V}, \quad V_{gmax} = 1.5 \text{ V}$$

Solution:

$$V_m = 24\sqrt{2} \quad R_1 \geq \frac{V_m}{I_{gmax}} = \frac{24\sqrt{2}}{12 \times 10^{-3}} = 2.8 \text{ k}\Omega \approx 3.3 \text{ k}\Omega$$


$$R \leq \frac{V_{gmax}R_1}{V_m - V_{gmax}} = \frac{1.5 \times 3.3 \times 10^3}{24\sqrt{2} - 1.5} = 145.8 \Omega \approx 120 \Omega$$

For finding R2  $\rightarrow$  
$$\frac{V_{gmin}}{V_m - V_{gmin}} = \frac{R}{R_1 + R_2}$$

$$R_2 = \frac{(V_m - V_{gmin})R}{V_{gmin}} - R_1 = \frac{(24\sqrt{2} - 0.6) \times 120}{0.6} - 3.3 \times 10^3 = 3.37 \text{ k}\Omega$$

(Drop across diode D is neglected)

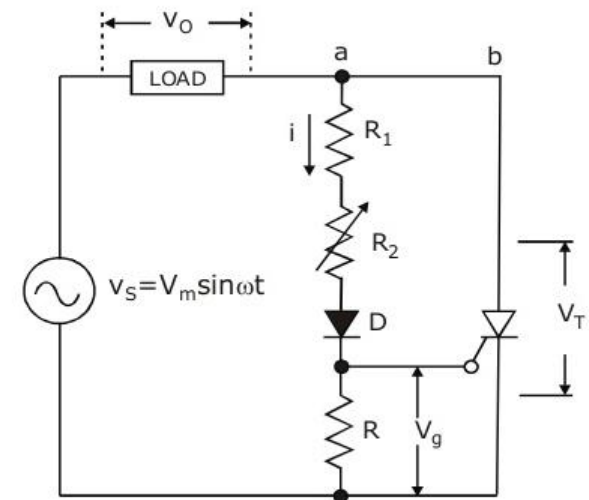Select 4.7 k Potentiometer for R<sub>2</sub>



# Problem

In a resistance firing circuit for SCR, the following parameters are applicable


$$I_{gt(\min)} = 0.5 \text{ mA},$$

$$V_{gt(\min)} = 0.7 \text{ V},$$


Supply voltage = 48 V, 50Hz

Resistance in gate current path = 70 k $\Omega$ .

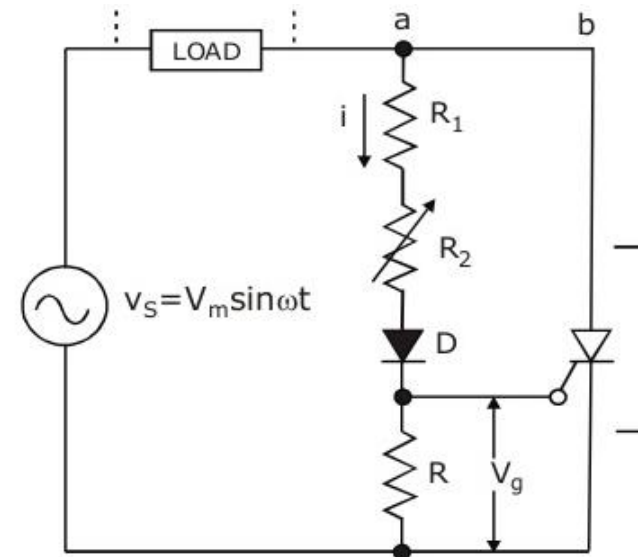- a) Find the firing angle for the above condition
- b) What is the resistance for which firing angle is 90 degrees



# Solution

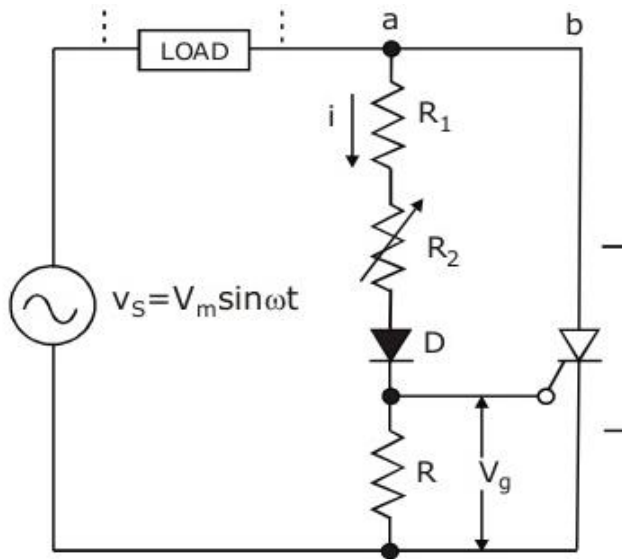

a)

$$\begin{aligned}
 e_t &= I_g \cdot (R_1 + R_2) + V_D + V_g \\
 &= 0.5 \times 10^{-3} \times 70 \times 10^3 + 0.6 + 0.7 \\
 &= 36.3 \text{ V}
 \end{aligned}$$

$$e_t = V_m \sin \omega t$$

$$36.3 = \sqrt{2} \times 48 \sin \omega t$$

$$\sin \omega t = \frac{36.3}{\sqrt{2} \times 48} = 0.535$$


$$\omega t = \sin^{-1} \omega t = 32.3^\circ$$

Firing angle = 32.3 degrees



# Solution

b)

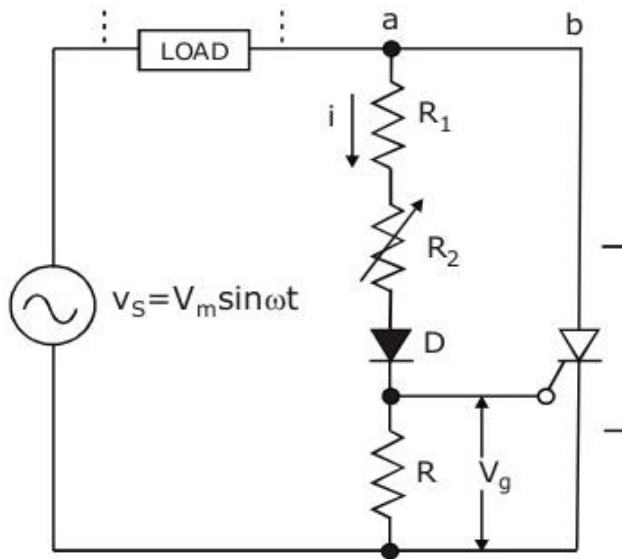


$$e_t = I_g \cdot (R_1 + R_2) + V_D + V_g$$
$$\sqrt{2} \times 48 = 0.5 \times 10^{-3} \times R + 0.6 + 0.7$$

$$66.6 = 0.5 \times 10^{-3} \times R$$

$$R = \frac{66.6}{0.5 \times 10^{-3}} = 133 \text{ k}\Omega$$

# RC Triggering Circuit

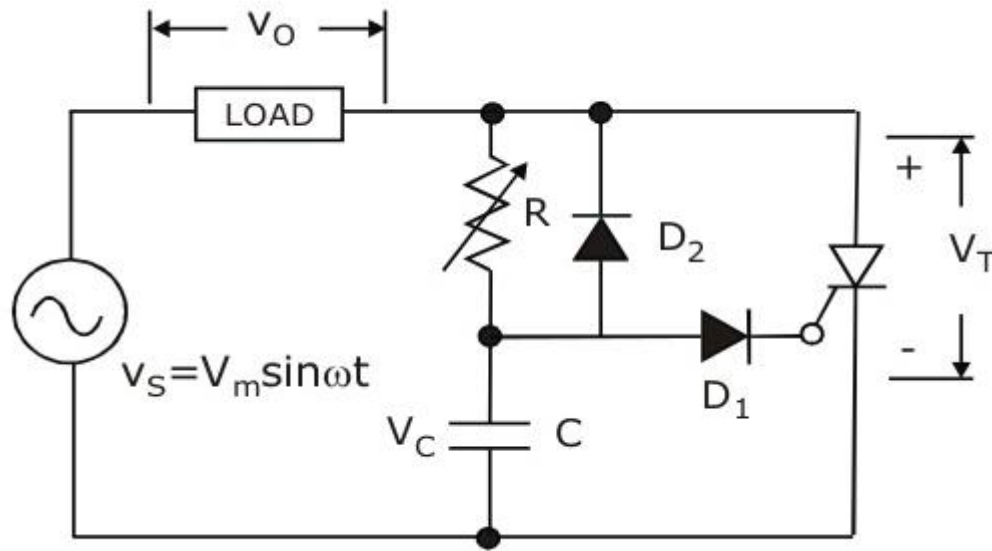

Advantage over R-triggering Circuit:  
**Controls upto 180 degrees**

$$RC \geq \frac{1.3 T}{2}$$



To ensure minimum gate current

$$v_s \geq R I_{g \min} + V_{g \min} + V_{D_1}$$

$$R \leq \frac{v_s - V_{g \min} - V_{D_1}}{I_{g \min}}$$


- ❑ Capacitor charges during the negative half cycle through  $D_2$
- ❑ When SCR is turned on, capacitor  $C$  is suddenly discharged through  $D_2$
- ❑  $D_1$  protects the SCR during negative half cycle

# RC Trig Waveforms

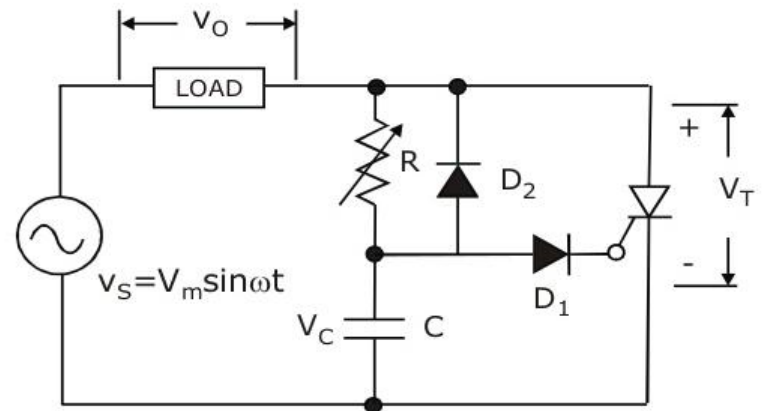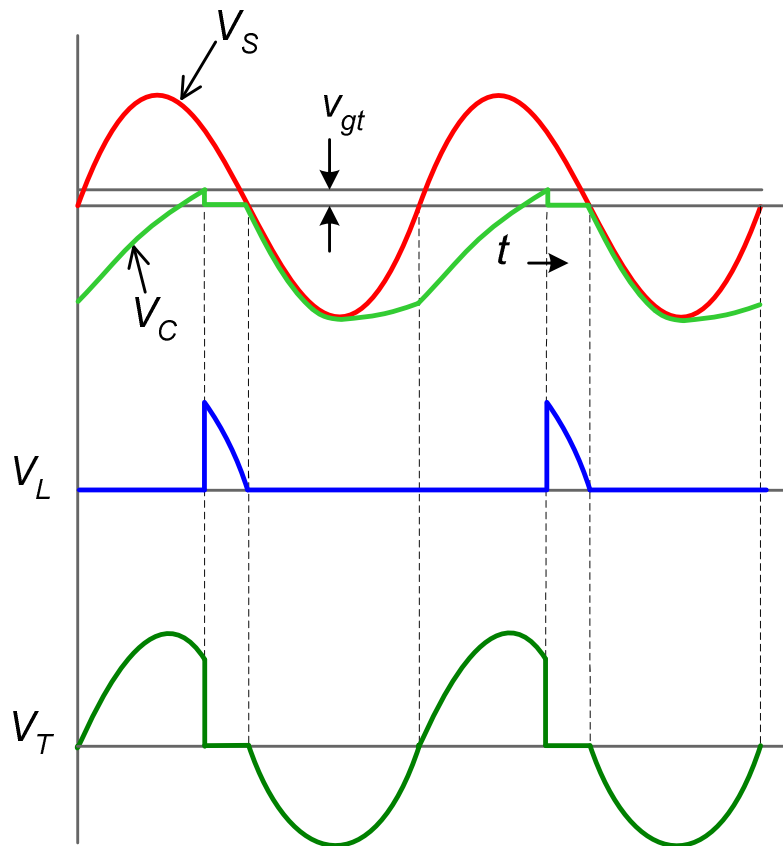


$$RC \geq \frac{1.3 T}{2}$$

# RC Full wave trigger circuit

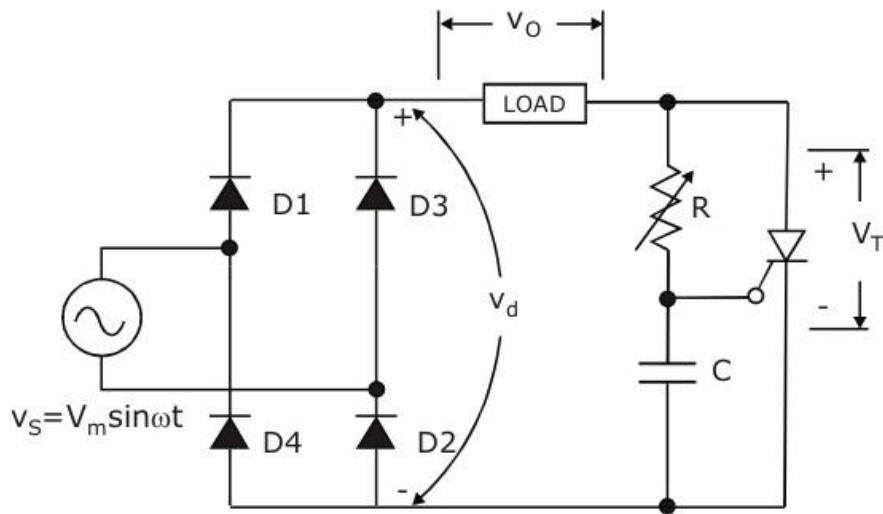


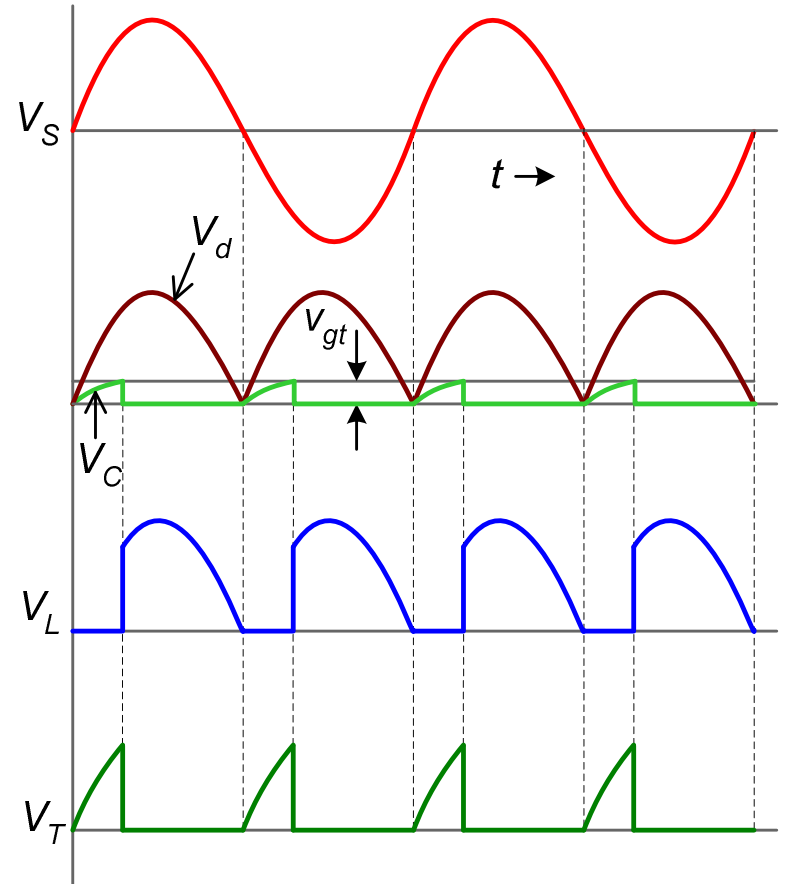- Initial Capacitor voltage in each half cycle is almost zero




$$RC \geq \frac{50 T}{2} \qquad R \leq \frac{v_s - V_{g \min}}{I_{g \min}}$$

# Unijunction Transistor (UJT)

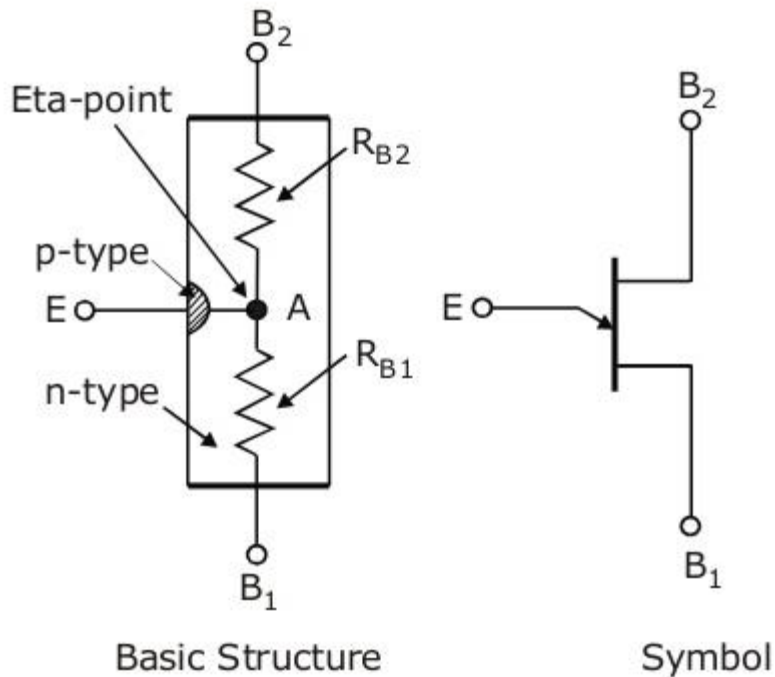

- ❑ Has a lightly doped n-type silicon layer to which a heavily doped p-type emitter is embedded
- ❑ The inter-base resistance is in the range of 5 – 10 kΩ
- ❑ This device cannot 'amplify'

# UJT Equivalent Circuit

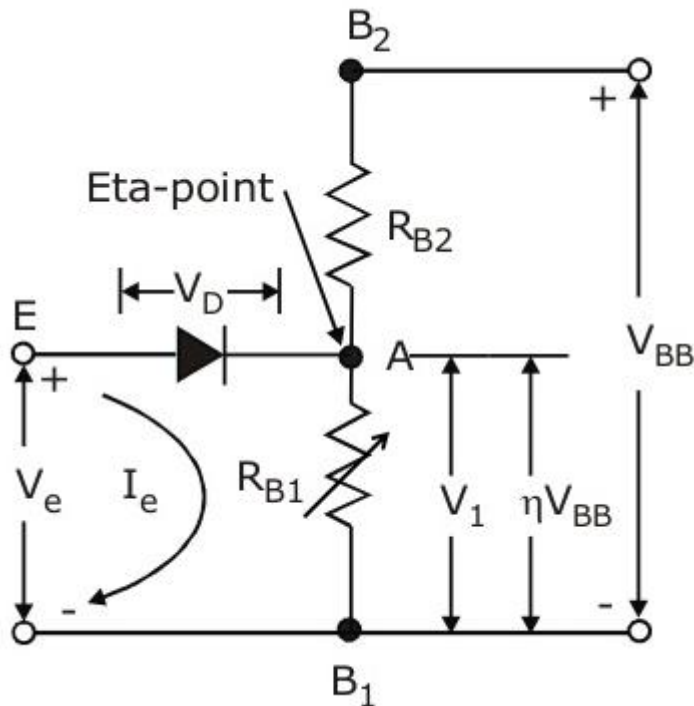


$$V_{AB_1} = \frac{R_{B_1}}{R_{B_1} + R_{B_2}} V_{BB} = \eta V_{BB}$$

$\eta$  is called **intrinsic standoff ratio**

Value of  $\eta$  varies from 0.5 – 0.8

- ❑ When  $V_e$  is more than  $V_1 + V_D$ , then the diode is forward biased and a current flows through  $R_{B_1}$
- ❑ Number of carriers in  $R_{B_1}$  increases and the resistance reduces
- ❑  $V_e$  decreases with increase in  $I_e$  and therefore the device is said to exhibit negative resistance

# UJT Characteristics

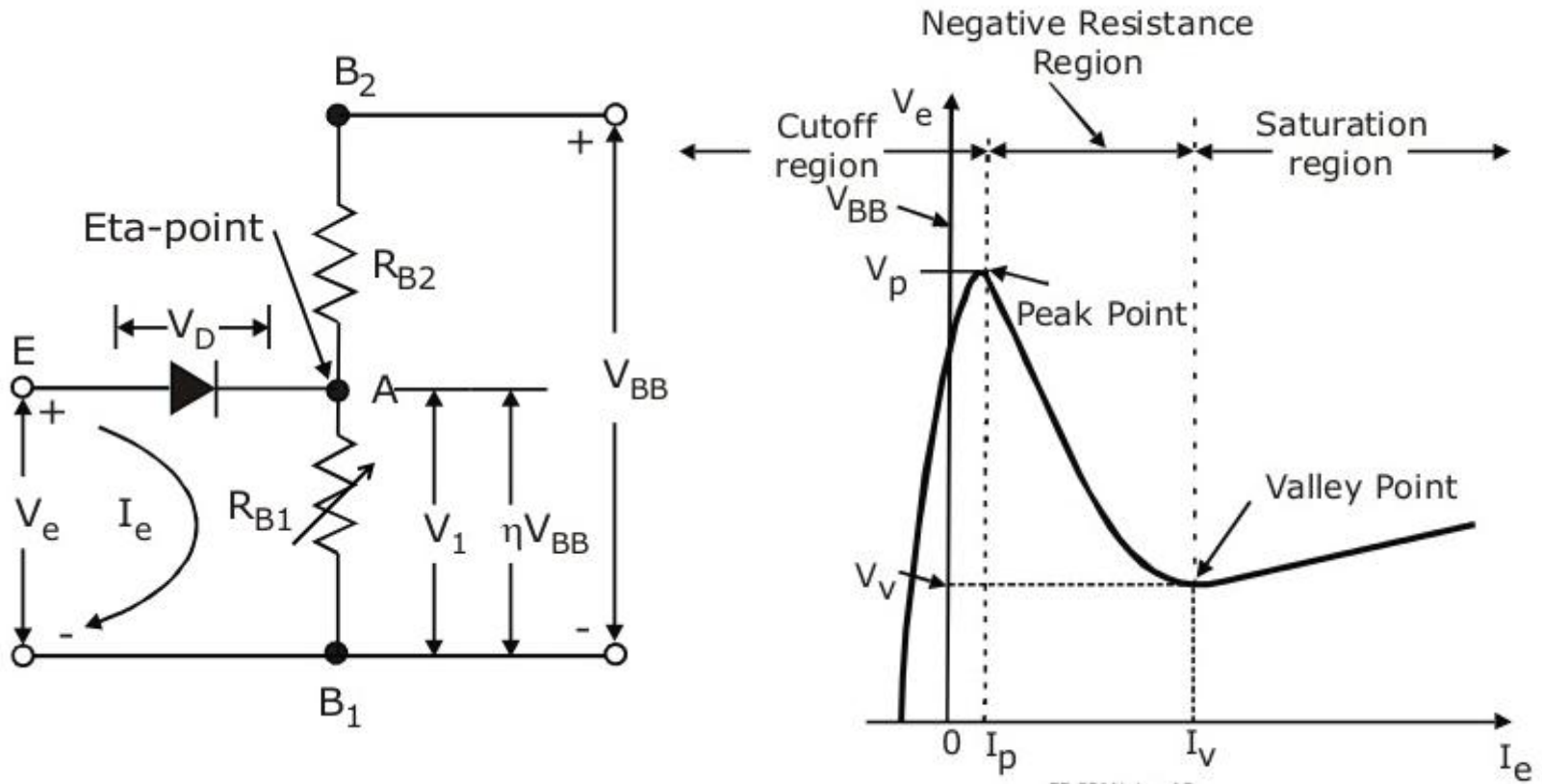

At peak point,  $V_e = V_1 + V_D$ ,

At Valley point,  $R_{B1}$  is minimum

# UJT parameters

---

## Maximum emitter reverse voltage

- Maximum reverse bias which the emitter – base2 junction can tolerate without breakdown. Typ: 30V

## Maximum inter-base voltage

- Maximum voltage possible between base1 and base2. Decided by the power dissipation. Typ: 35 V

## Interbase resistance

- Typ: 4.7 k – 9.1 k

## Intrinsic stand off ratio

- Typ: 0.56 – 0.75

## Maximum peak emitter current

- Typ : 2A


## Emitter leakage current

- The emitter current when  $V_e$  is less than  $V_p$  and the UJT is off.
- Typ 12  $\mu$ A

*Typical values are of 2N2646*



# UJT Oscillator

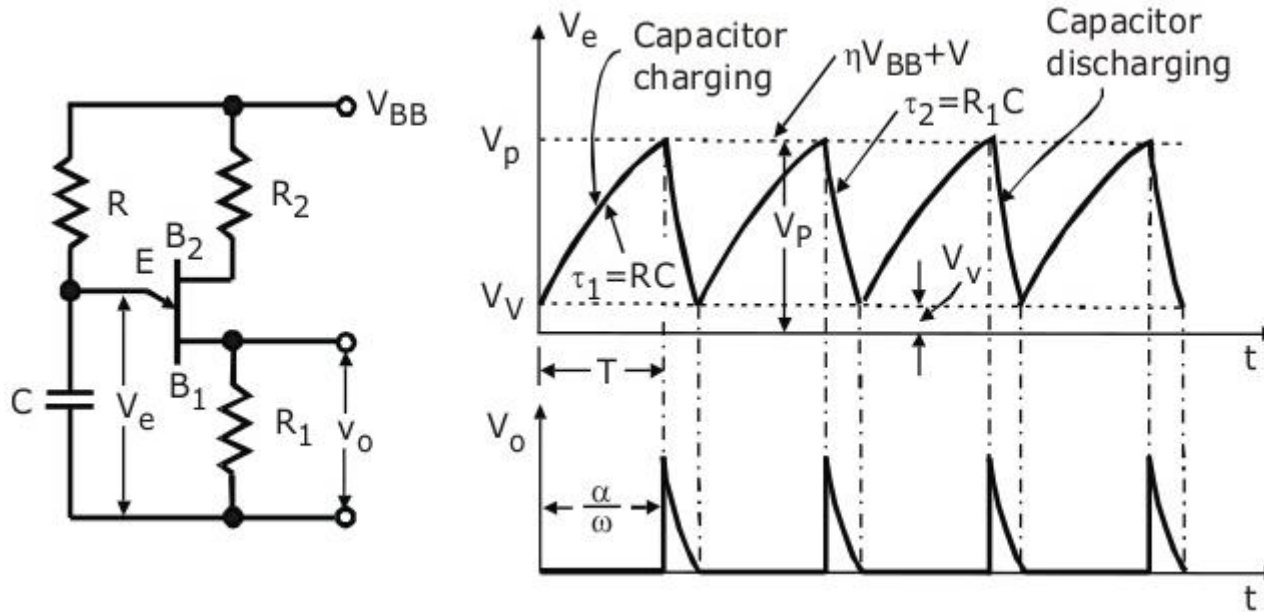

- $R_1$  and  $R_2$  are much less than the inter-base resistance
- The output pulses can be used to trigger an SCR

# Design

$$V_C = V_{BB} \left( 1 - e^{-t/RC} \right)$$



Time required for C to charge from  $V_v$  to  $V_p$  is obtained as follows

$$V_p = \eta V_{BB} + V_D = V_v + V_{BB} \left( 1 - e^{-t/RC} \right)$$

Assuming  $V_D = V_v$       $\eta = \left( 1 - e^{-t/RC} \right)$

For this case,  $t \cong T$
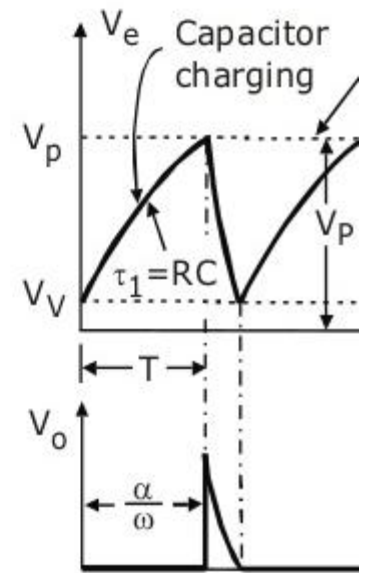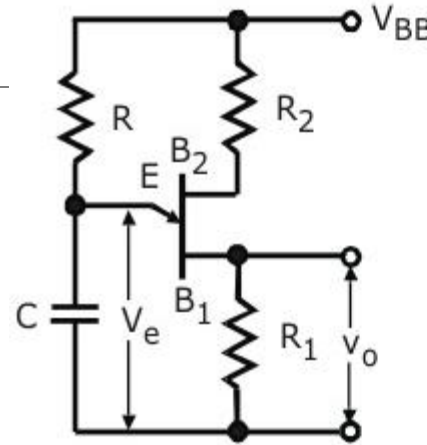
$$T = \frac{1}{f} = RC \ln \left( \frac{1}{1-\eta} \right)$$




$R_1$  is selected based on voltage level required to trigger the SCR



$R_2$  is selected using the empirical formula:

$$R_2 = \frac{10^4}{\eta V_{BB}}$$

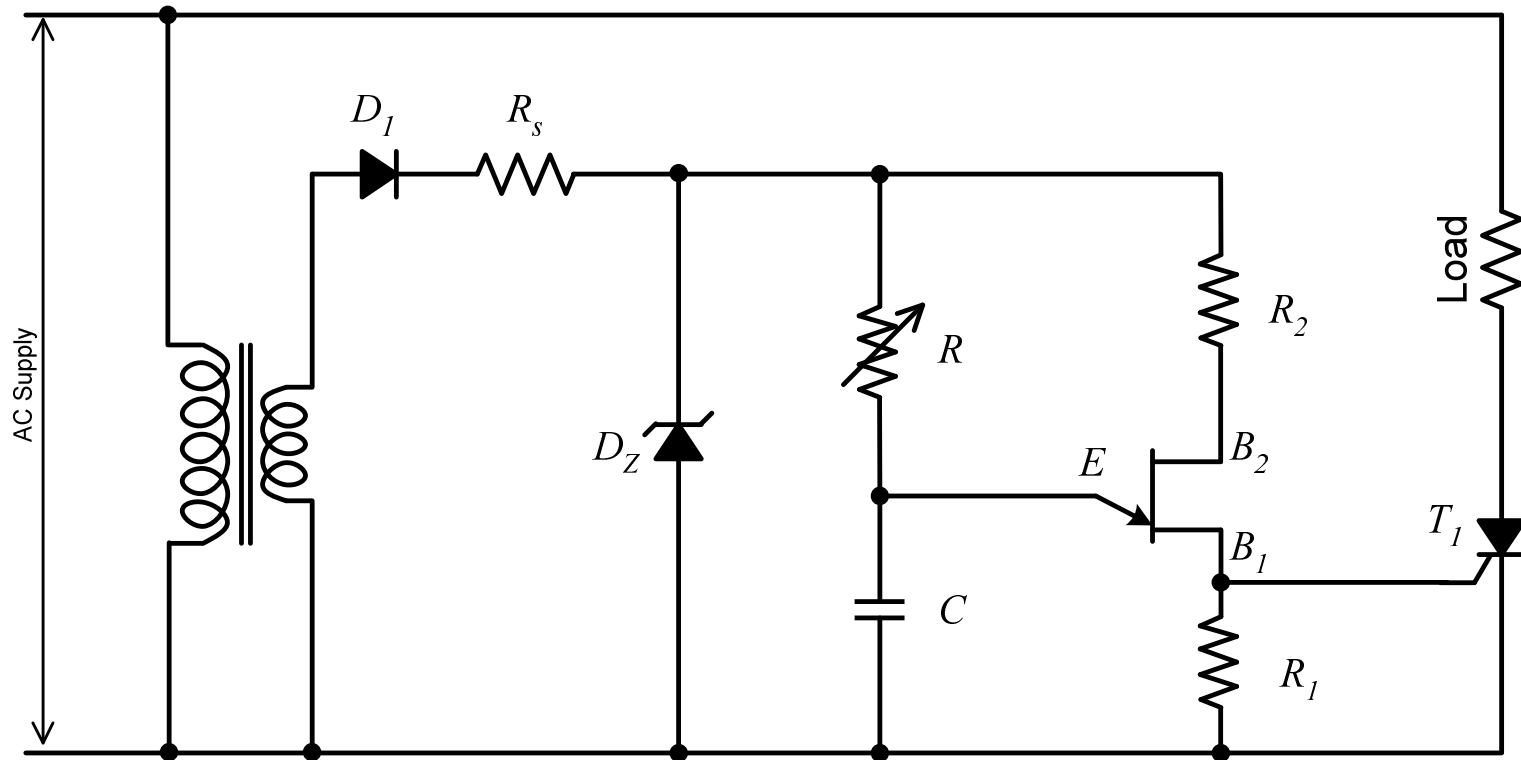
# UJT firing circuit for Half Wave Controller



# Waveforms for Half Wave Controller

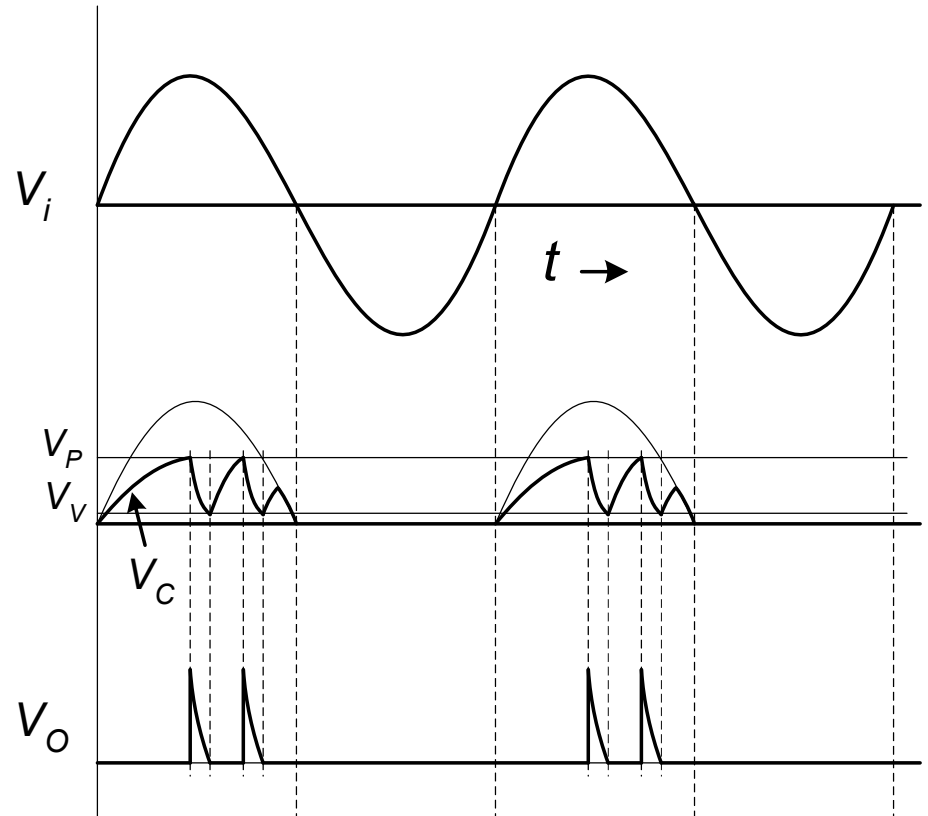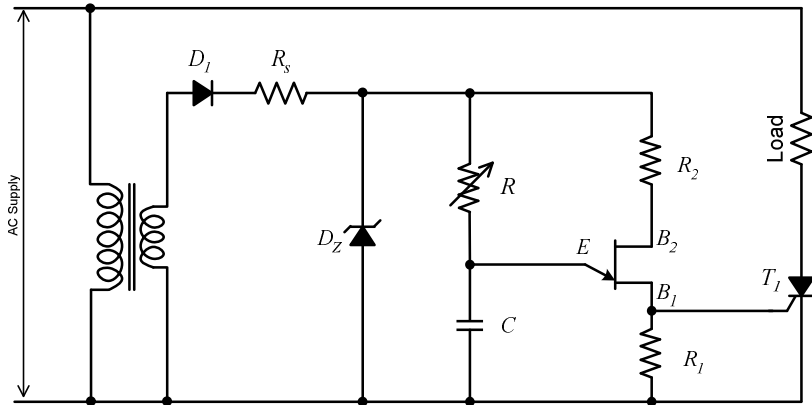

# Full wave UJT trigger Circuit

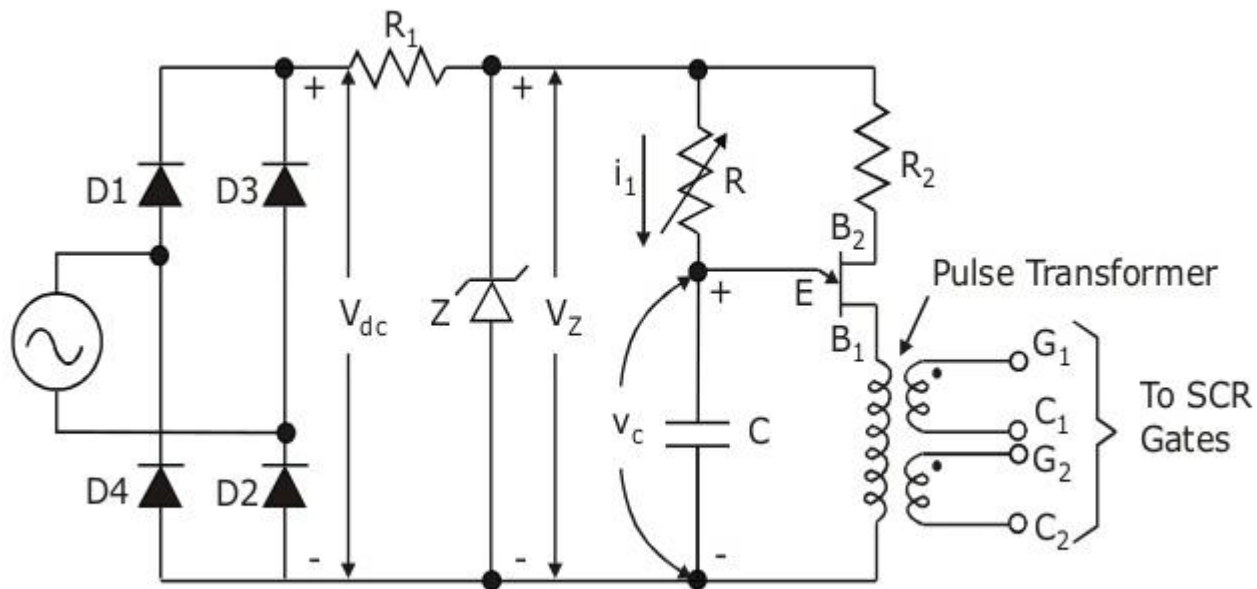

# Problem

Design a UJT relaxation oscillator using UJT2646 for triggering an SCR. The UJT has the following parameters

$$\eta = 0.63, V_{BB} = 20 \text{ V}, V_P = 13.2 \text{ V}, I_P = 50 \mu\text{A}$$

$$V_V = 2 \text{ V}, I_V = 6 \text{ mA}, R_{BB} = 7 \text{ k}\Omega, \text{leakage current} = 2.5 \text{ mA}$$


Also find the minimum and maximum time period of oscillation.

## Solution:

Assume  $C = 0.1 \mu\text{F}$

$$R_{\max} = \frac{V_{BB} - V_P}{I_P} = \frac{20 - 13.2}{50 \times 10^{-6}} = 136 \text{ k}\Omega$$
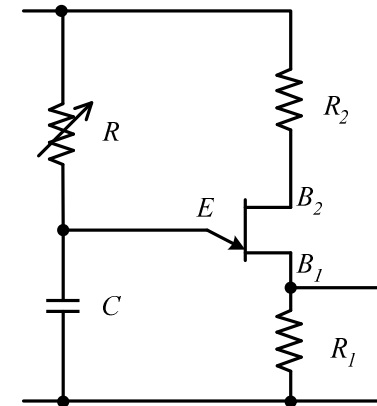
$$R_{\min} = \frac{V_{BB} - V_V}{I_V} = \frac{20 - 2}{6 \times 10^{-3}} = 3 \text{ k}\Omega$$




---

Approximate value of  $R_2 = \frac{10^4}{\eta V_{BB}} = \frac{10^4}{0.63 \times 20} = 794 \Omega$

$$R_1 = \frac{V_{gmin}}{\text{Leakage current}} = \frac{0.7}{2.5 \times 10^{-3}} = 280 \Omega$$



$$T_{\max} = RC \ln\left(\frac{1}{1-\eta}\right) = 136 \times 10^3 \times 0.1 \times 10^{-6} \times \ln\left(\frac{1}{1-0.63}\right) = 13.5 \text{ ms}$$
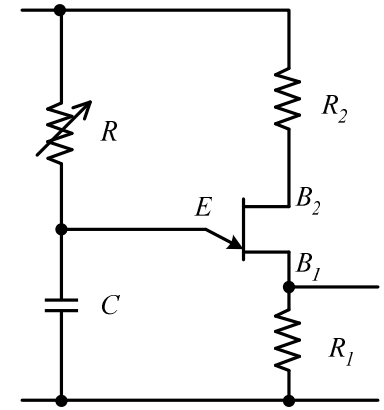
$$T_{\min} = 3 \times 10^3 \times 0.1 \times 10^{-6} \times \ln\left(\frac{1}{1-0.63}\right) = 0.3 \text{ ms}$$



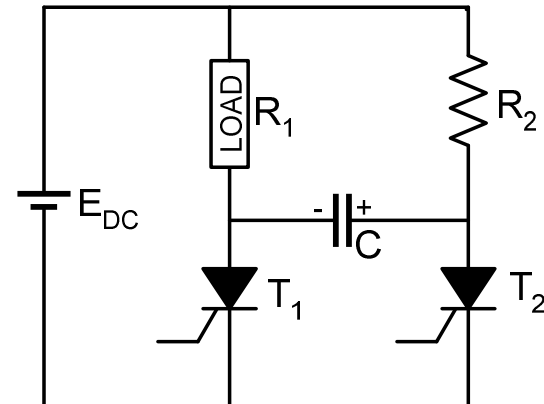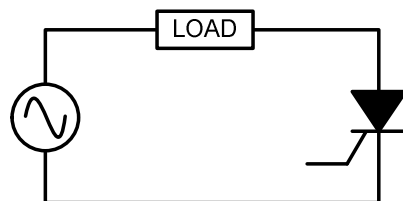
# Commutation

- ❑ Commutation is the process by which a thyristor is turned off or current diverted to another path.
- ❑ There are two types of commutation
  - Natural Commutation
  - Forced Commutation
- In natural commutation, the reversing nature of alternating voltages turn off the thyristor
- Suitable for AC circuits only
- Current passes through a zero in every half cycle
- No external circuit is required for natural commutation
- In DC circuits, external circuits are necessary for turn off of thyristors
- Turn off with external circuits is called forced commutation






# Pulse Transformer

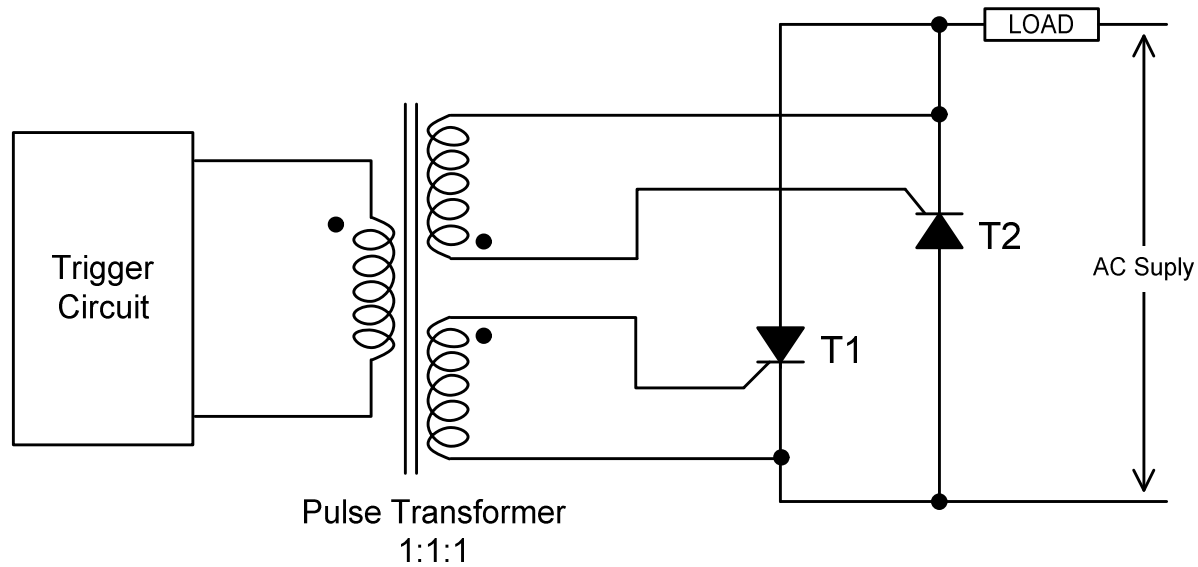

- ❑ Used to trigger SCR, TRIAC etc
- ❑ Provides Electrical isolation between power circuit and control circuit

# Optical Isolation

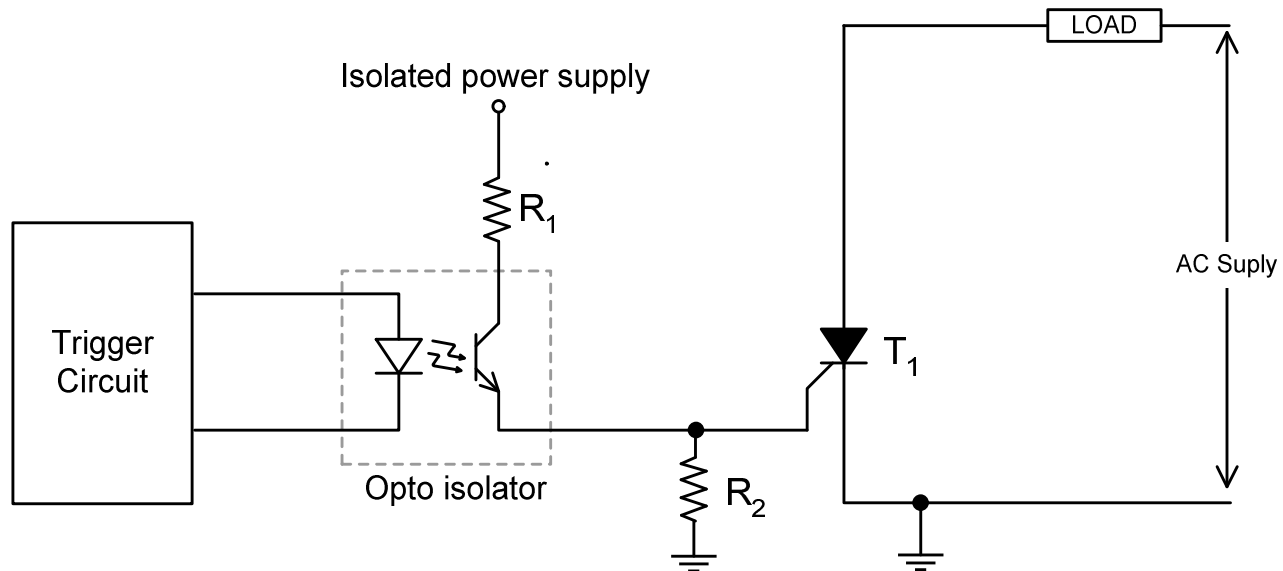

- ❑ Used to trigger SCR, TRIAC etc
- ❑ Provides Electrical isolation between power circuit and control circuit