

Power Electronics


CHOPPERS

2018



Dr. Francis M. Fernandez

Choppers

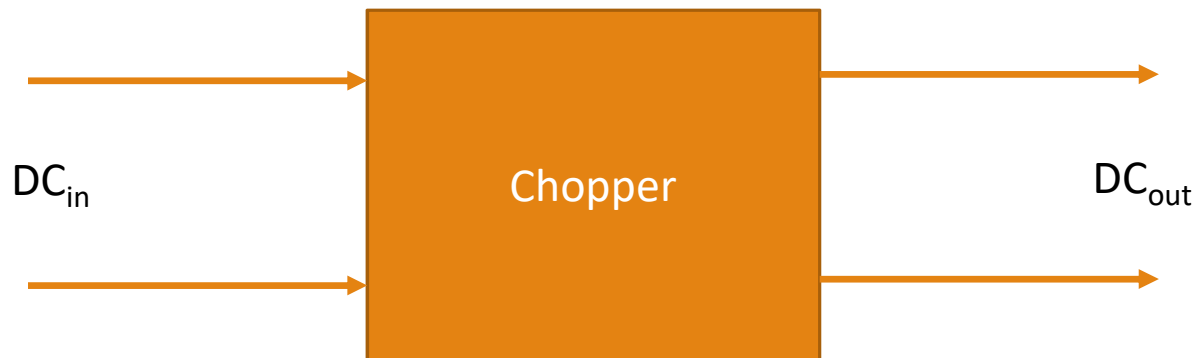- ❑ It is a DC-DC converter
- ❑ It can be **step up** chopper or **step down** chopper



Step-down Chopper (Buck converter)

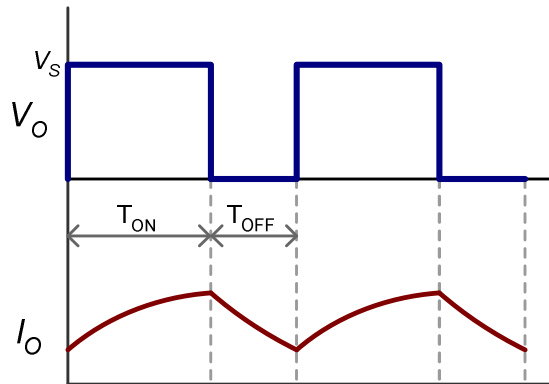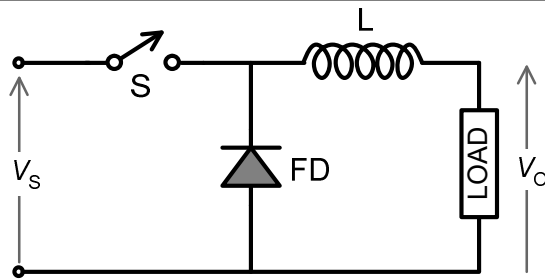



$$\text{Average output, } V_o = V_s \frac{T_{ON}}{T_{ON} + T_{OFF}} = V_s \times \alpha$$

$$\alpha \text{ is the } \textit{duty cycle}, \text{ which is equal to } \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$V_{O(RMS)} = \sqrt{V_s^2 \frac{T_{ON}}{T_{ON} + T_{OFF}}} = \sqrt{V_s^2 \times \alpha} = V_s \sqrt{\alpha}$$

- ❑ Switching is done at **chopping frequency**, typically 5 kHz to 25 kHz
- ❑ SCR, GTO, BJT, MOSFET or IGBT can be used as switch
- ❑ MOSFET and IGBT are preferred as switch for common applications since special commutation circuits are not required.


Step-up Chopper (Boost Converter)

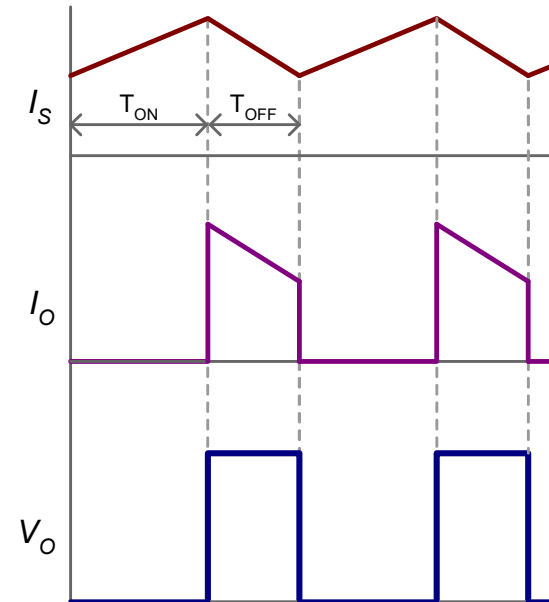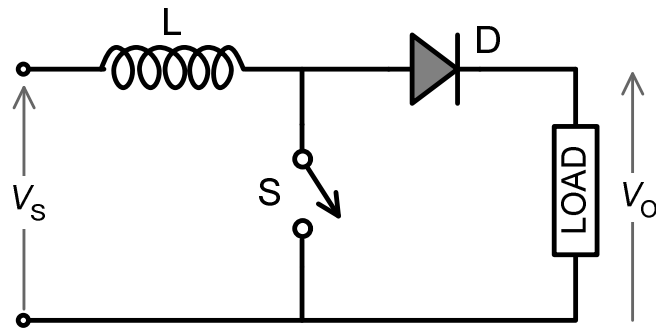

$$\text{Average output, } V_o = V_s \frac{1}{1-\alpha}$$

$$\alpha \text{ is the duty cycle, which is equal to } \frac{T_{ON}}{T_{ON} + T_{OFF}}, \text{ ie } \alpha = \frac{T_{ON}}{T}$$

Buck-Boost Converter

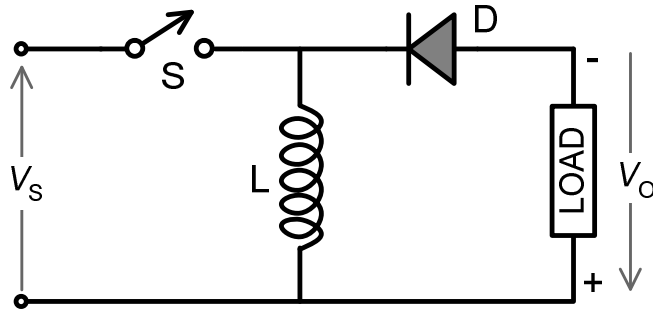

$$\text{Average output, } V_o = V_s \frac{\alpha}{1-\alpha}$$

$$\alpha \text{ is the duty cycle, } \alpha = \frac{T_{ON}}{T}$$


- Output polarity is different when compared to buck or boost converter
- For $0 < \alpha < 0.5$ step down operation is achieved
- For $0.5 < \alpha < 1.0$ step up operation is achieved

Control Strategies

Time Ratio Control


PWM Control

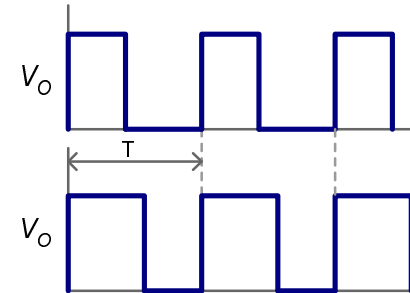(Frequency is constant and pulse width is controlled)




Variable Frequency Control

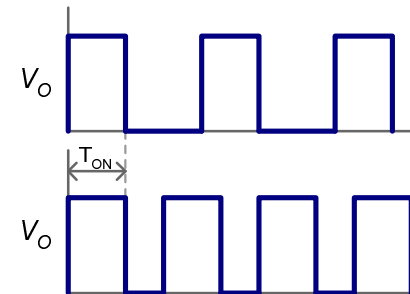(Pulse width is constant and frequency is controlled)



Current Limit Control

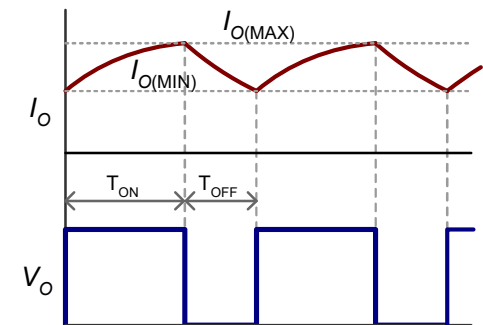(Switching is done at upper limit and lower limit of output current)



Example



A DC chopper connected to a 120 V source supplies to an inductive load of 30 mH in series with a 6 Ω resistance. A freewheeling diode is connected across the load. The load current varies between 10A and 12A. Determine the duty cycle of chopper.

$$\text{Average value of load current} = \frac{10+12}{2} = 11 \text{ A}$$

$$\text{Maximum value of load current} = \frac{120}{6} = 20 \text{ A}$$

$$\text{Average value of output voltage} = 120 \times \frac{11}{20} = 66 \text{ V}$$
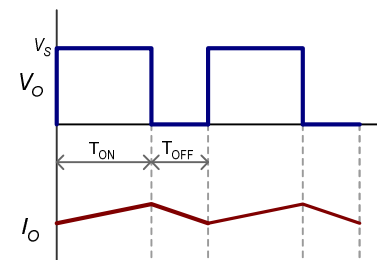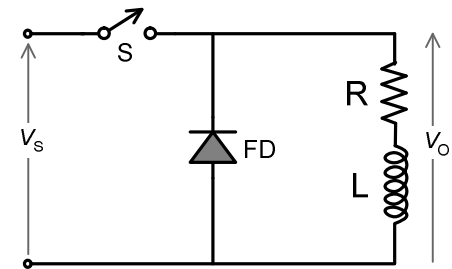
$$\text{Duty Cycle} = \frac{T_{ON}}{T_{ON} + T_{OFF}} = \frac{V_O}{V_S} = \frac{66}{120} = 0.55$$



Example

A step-up chopper is used to generate 220 V from 100 V dc source. The blocking period of switch is $80\mu\text{s}$. Compute the required pulse width.

$$\text{Output voltage, } V_o = V_s \frac{1}{1 - \alpha}$$

$$220 = 100 \frac{1}{1 - \alpha}$$



$$\text{then, } \alpha = 0.5454$$

$$\text{Duty cycle, } \alpha = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$0.5454 = \frac{T_{ON}}{T_{ON} + 80}$$





$$T_{ON} = 96 \mu\text{s}$$

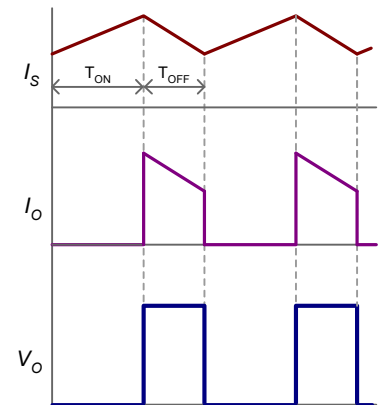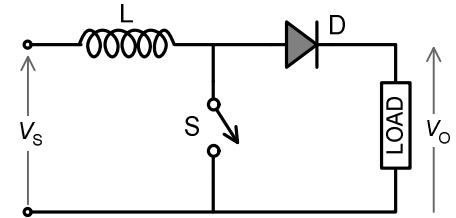

Chopper Classification



Type ->	Class A	Class B	Class C	Class D	Class E
Quadrants					
Output Polarity	Voltage: + Current: +	Voltage: + Current: -	Voltage: + Current: ±	Voltage: ± Current: +	Voltage: ± Current: ±
Typical Application	DC Motor operation	Regenerative braking of DC motor	Both motoring and regenerative braking of DC motor	Both motoring and regenerative braking of DC motor	Reversible regenerative motor drive

Type A Chopper

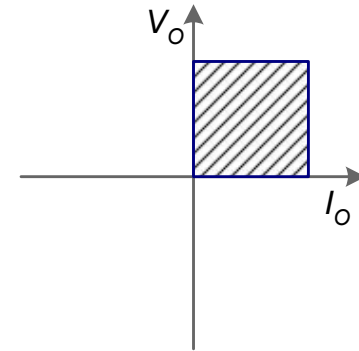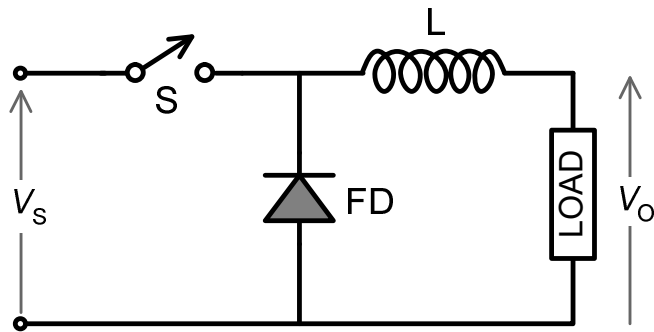

- ❑ Average value of both voltage and current are **positive**
- ❑ This chopper is also called **step down chopper**
- ❑ Freewheeling diode FD maintains the current when switch S is off
- ❑ Power flow is always from Source to Load

Type B Chopper


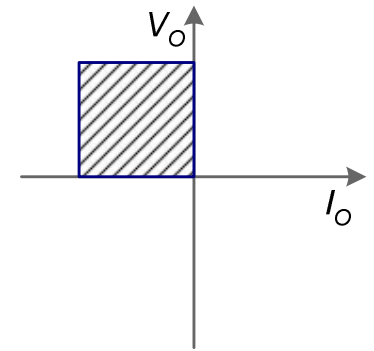
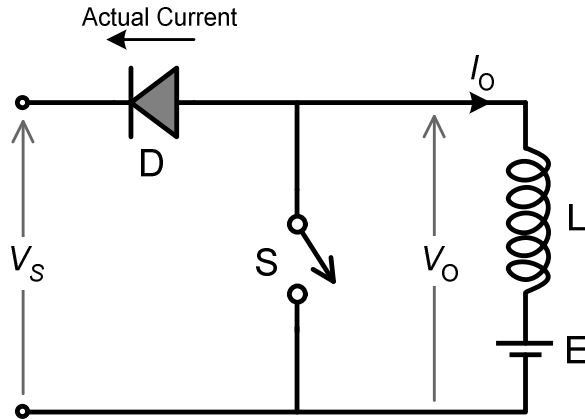


$$\text{Load voltage, } V_o = E + L \frac{di}{dt}$$

V_o may be more than V_s and make diode D forward biased

- ❑ The load should have a battery source or it may be a motor which has back emf
- ❑ Average value of **voltage is positive** but **current is negative**
- ❑ This chopper is also called **step up chopper**
- ❑ Power flow is from Load to Source


Type C Chopper

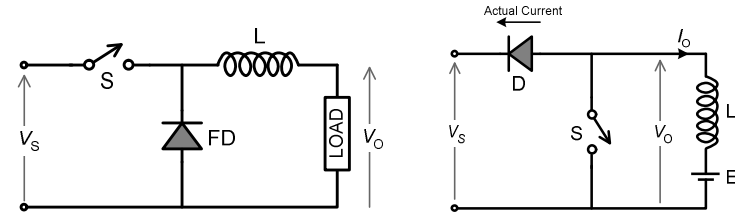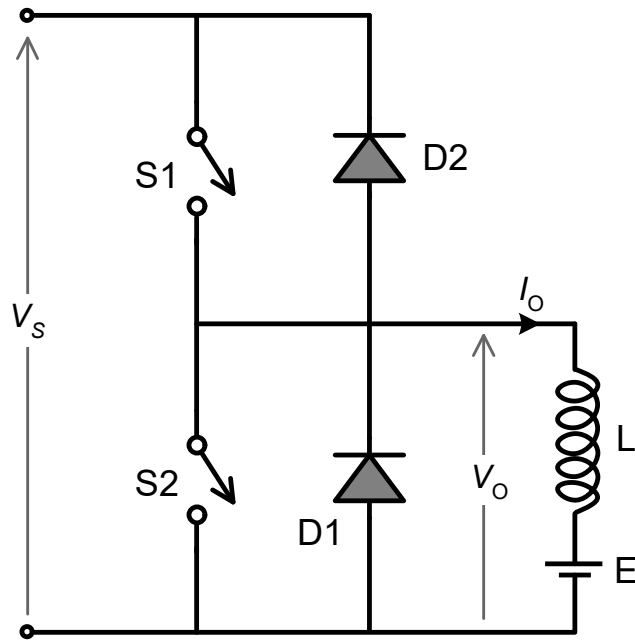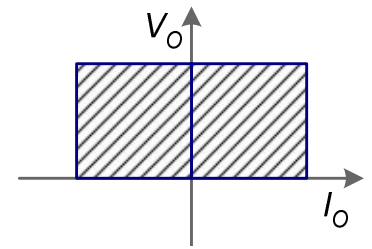


Is a combination of
Type A and Type B Choppers

- ❑ Average value of voltage is **positive** but current may be **positive or negative**
- ❑ Switches S1 and S2 should not be turned on at the same time
- ❑ Power flow may be in either direction
- ❑ Used for motoring and regenerative braking of dc motors


Type C operating modes

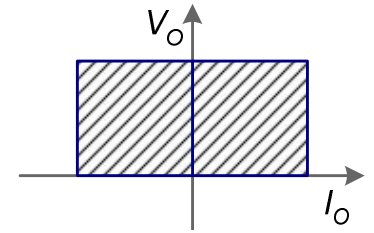



Type A operation:

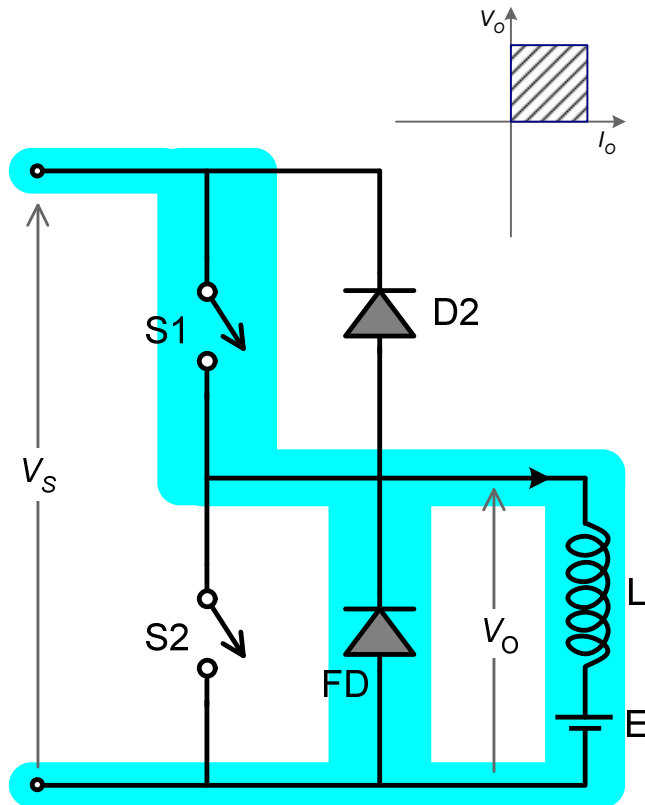

Type B operation:



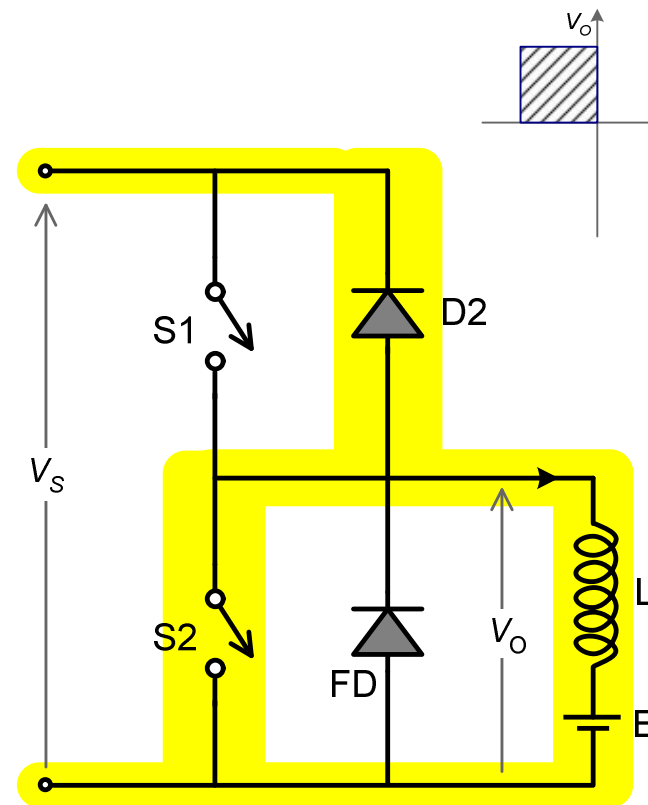


Type C Waveforms

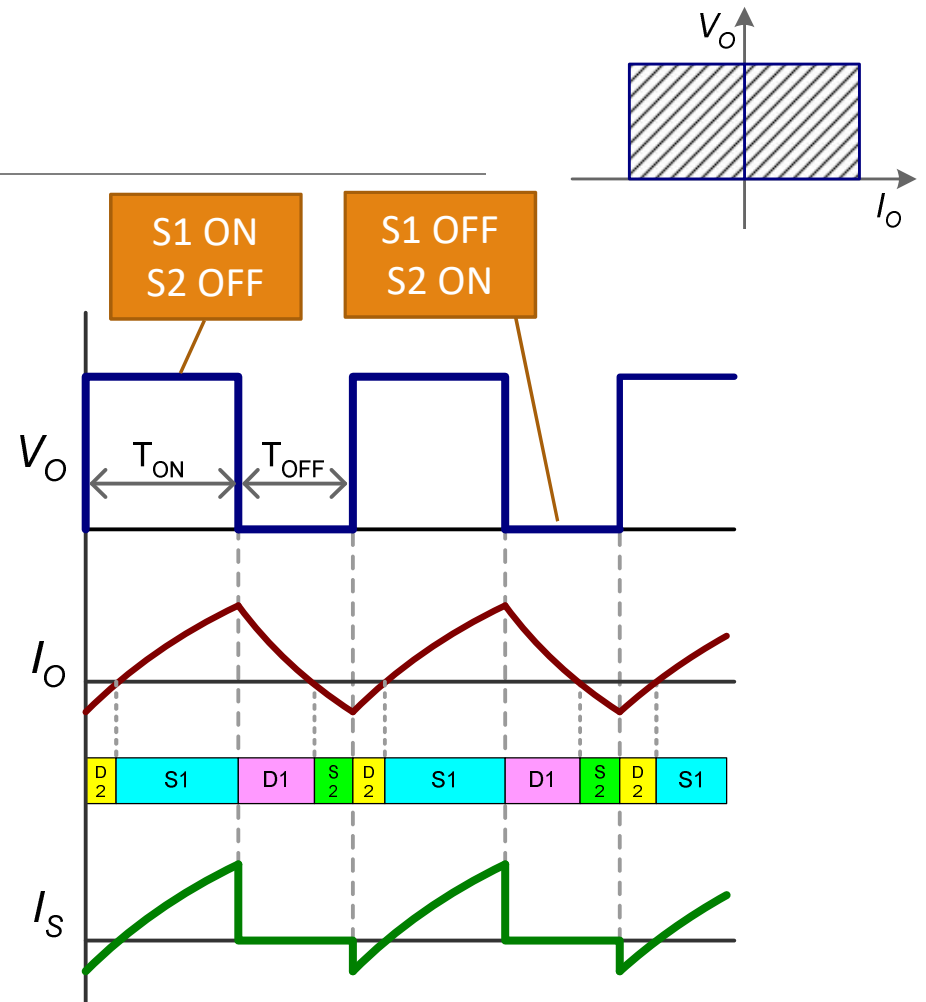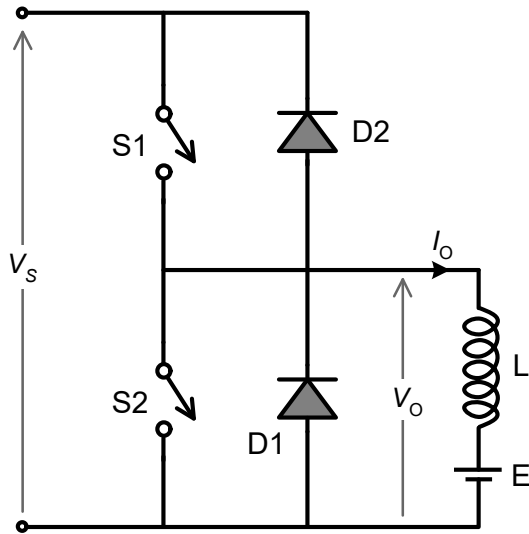





- Depending on duty cycle, the average value of load current I_o may be either positive or negative

Type D Chopper

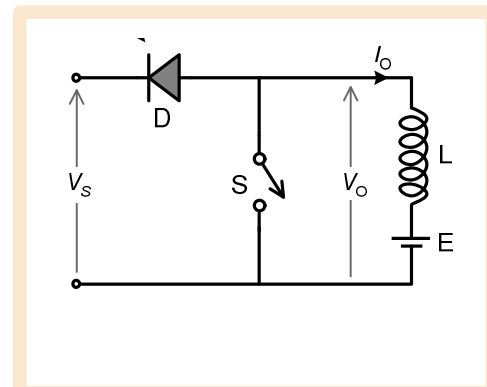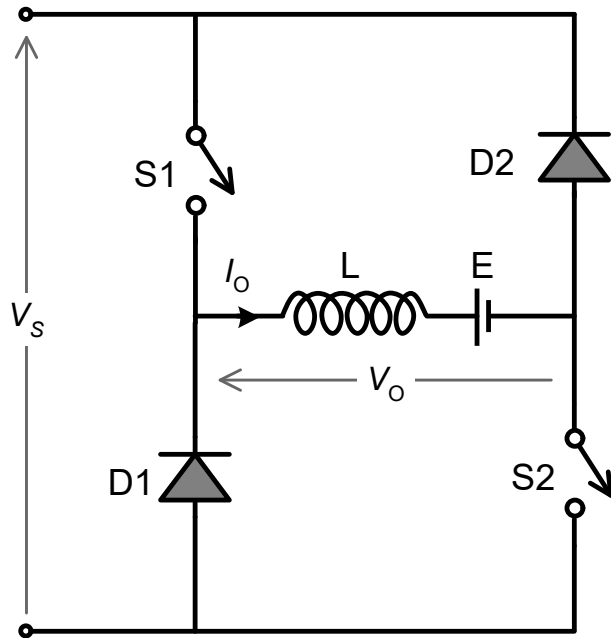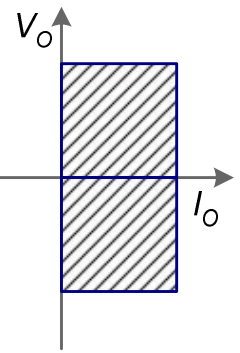


Is a combination of two Type B Choppers

Type D Operation

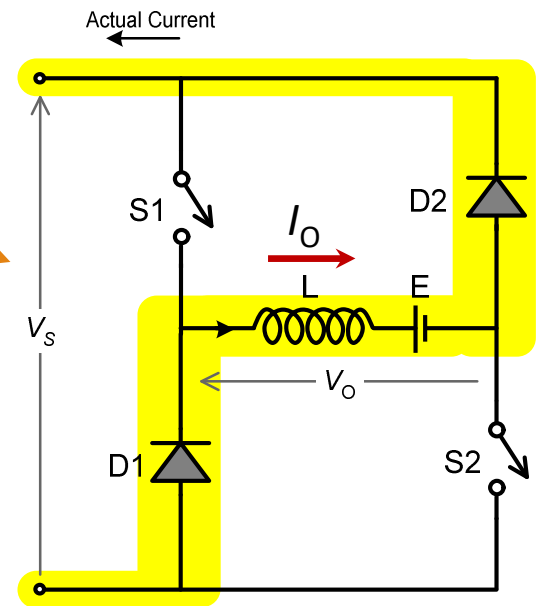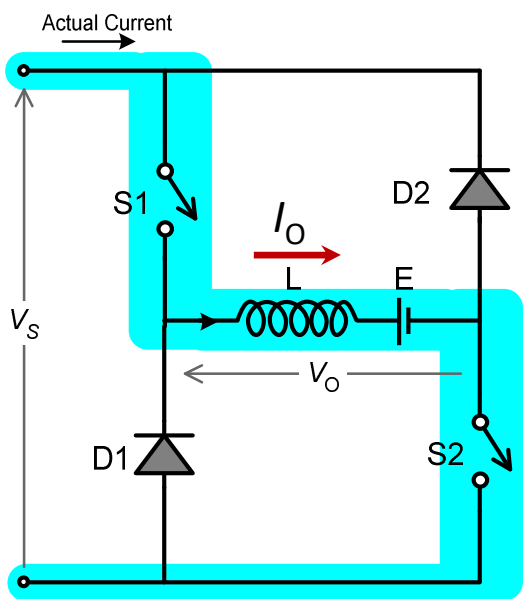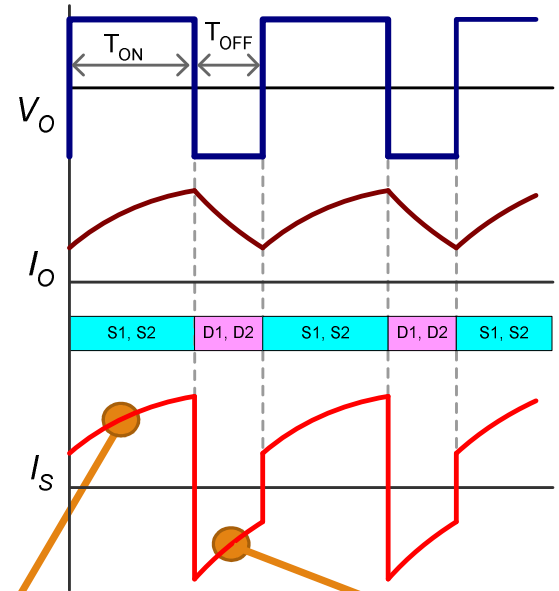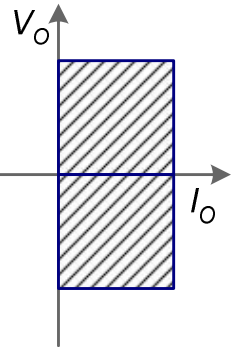


Direction of load current I_o is the same

Type D Waveforms

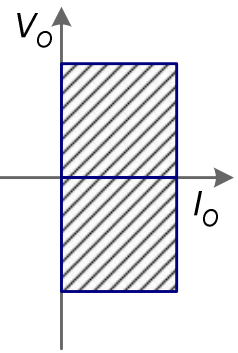


$$T_{ON} > T_{OFF}$$

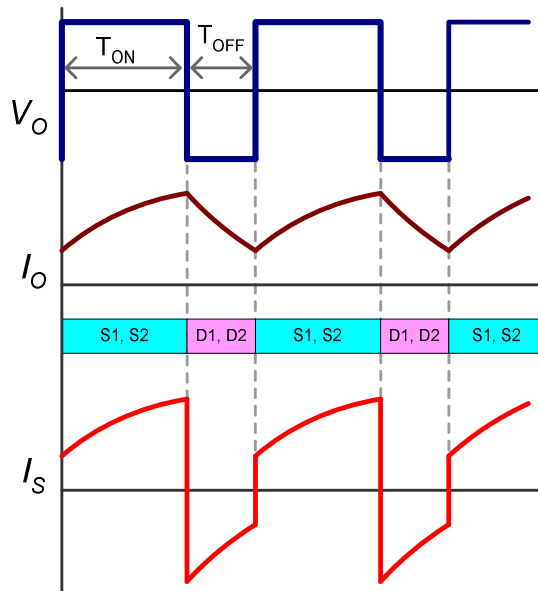




Average voltage is positive and output current is also positive; so **first quadrant** operation

$$T_{ON} < T_{OFF}$$

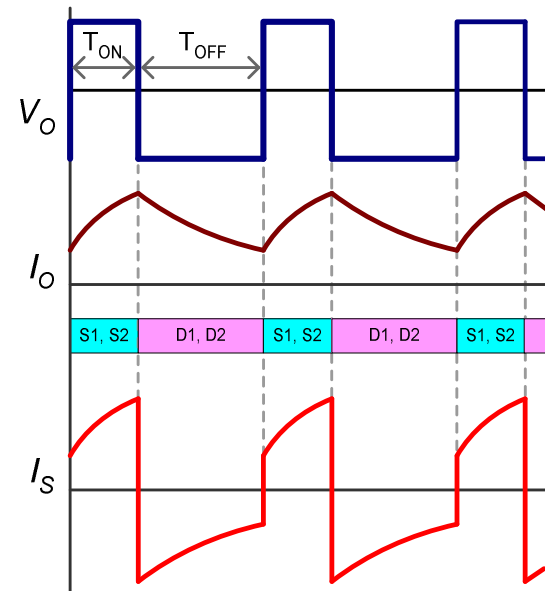



Average voltage is negative and output current is positive; so **fourth quadrant** operation

Type E Chopper

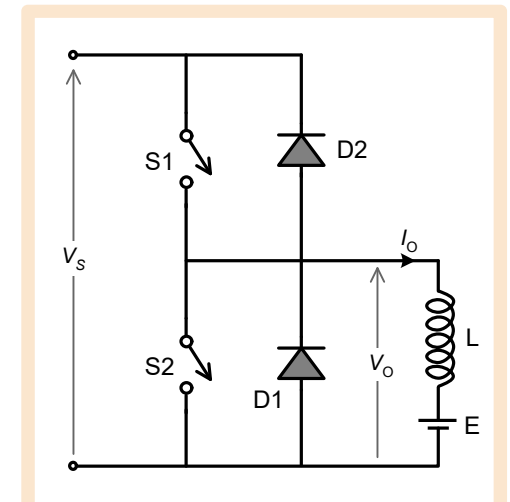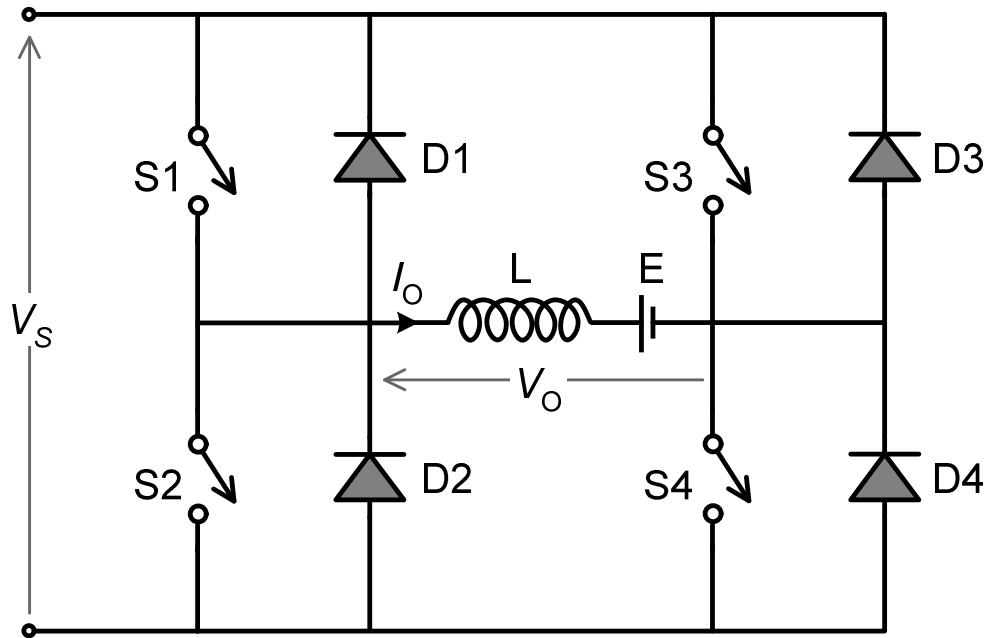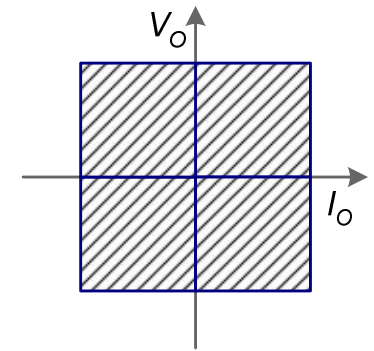

Is a combination of **two Type C Choppers**



Type E Chopper – in Q1

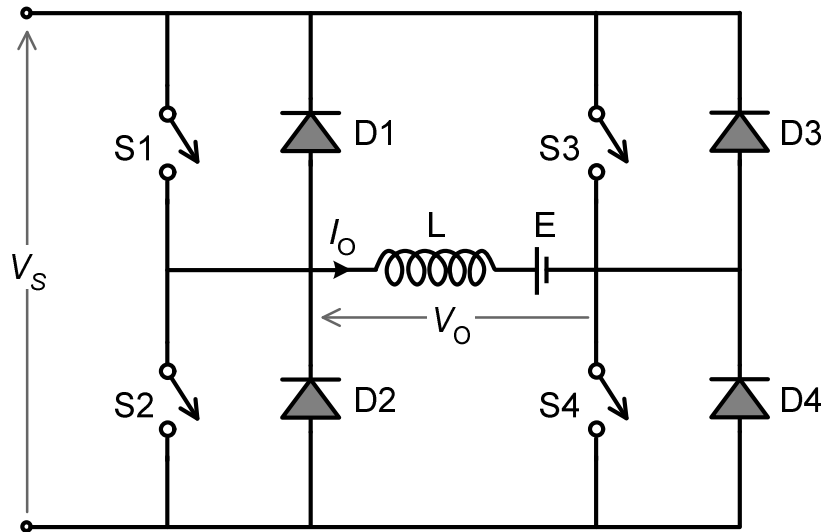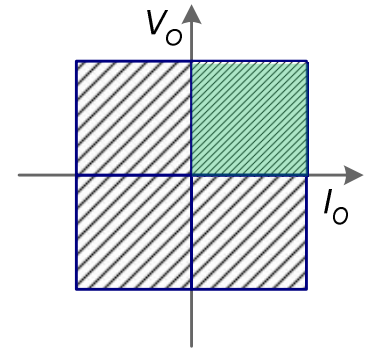

First Quadrant Operation

Common Condition	Operation	Current flow	Action
S2, S3 off, S4 is kept on	S1 is turned on	through S1, L, E and S4	Energy stored in Inductor L
	S1 is turned off	through D2, L, E and S4	Freewheeling current flows



Type E Chopper – in Q2

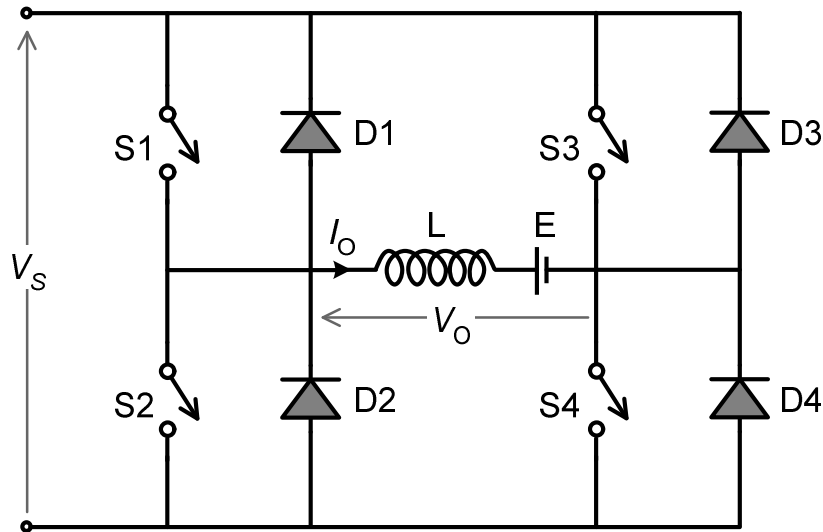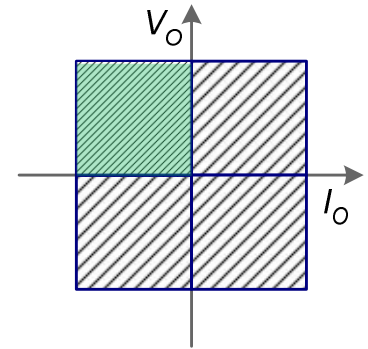

Second Quadrant Operation

Common Condition	Operation	Current flow	Action
S1, S3 and S4 are kept off	S2 is turned on	through L, S2, D4 and E	Energy stored in Inductor L
	S2 is turned off	through D1, L, E and D4	Current fed back to source

Type E Chopper – in Q3

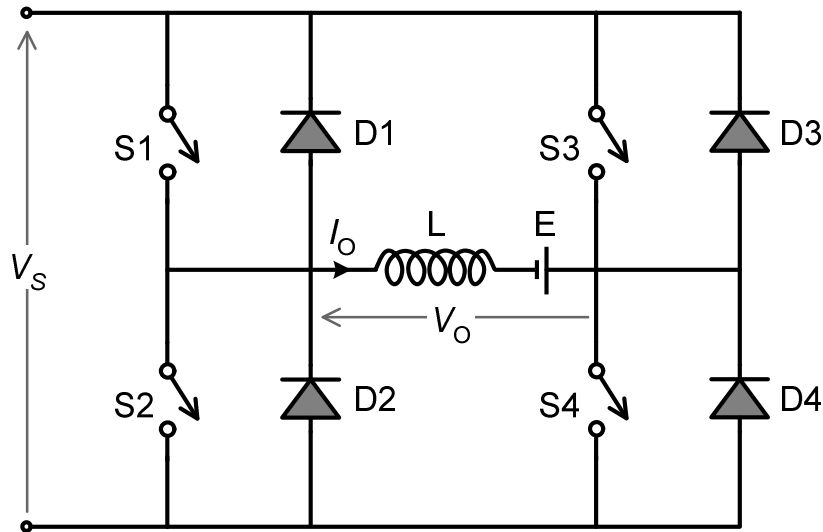
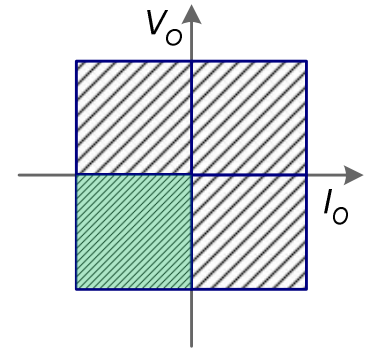


Polarity of E is reversed here

Third Quadrant Operation

Common Condition	Operation	Current flow	Action
S1, S4 off, S2 is kept on	S3 is turned on	through S3, E, L and S2	Energy stored in Inductor L
	S3 is turned off	through L, S2, D4 and E	Freewheeling current flows

Type E Chopper – in Q4

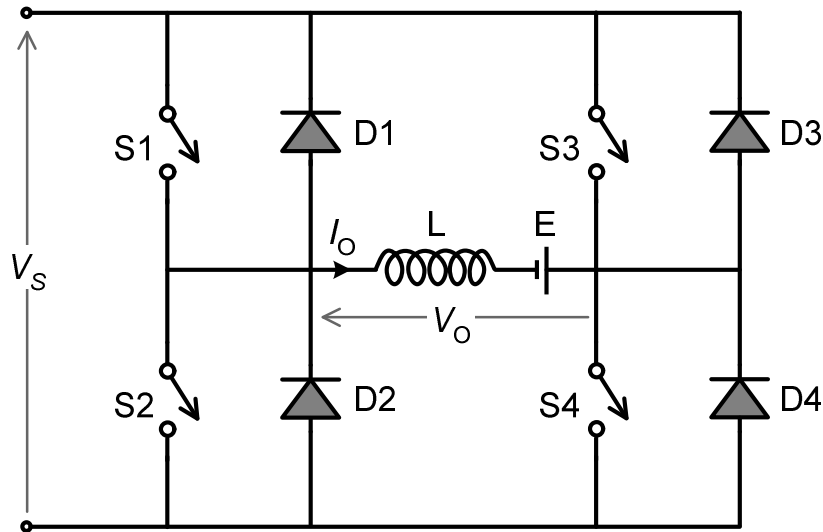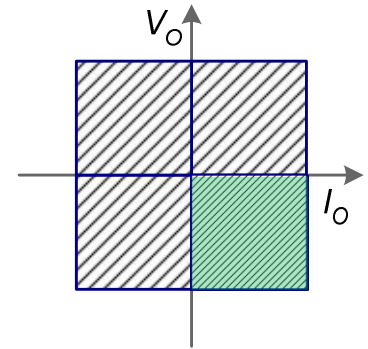



Polarity of E is reversed here

Fourth Quadrant Operation



Common Condition	Operation	Current flow	Action
S1, S2 and S3 are kept off	S4 is turned on	through S4, D2, L and E	Energy stored in Inductor L
	S4 is turned off	through D3, E, L and D2	Current fed back to source

Switching Regulators

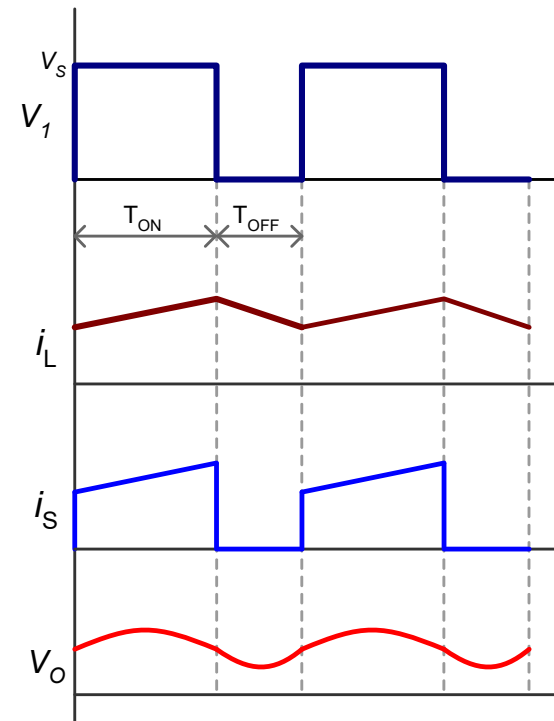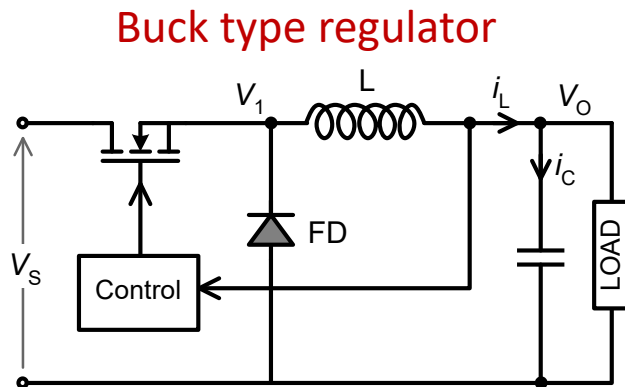- ❑ Switching regulators are used to convert an unregulated DC voltage to regulated DC voltage
- ❑ Buck, Boost and Buck-boost type are available
- ❑ Efficient compared to linear regulators



Filter Design

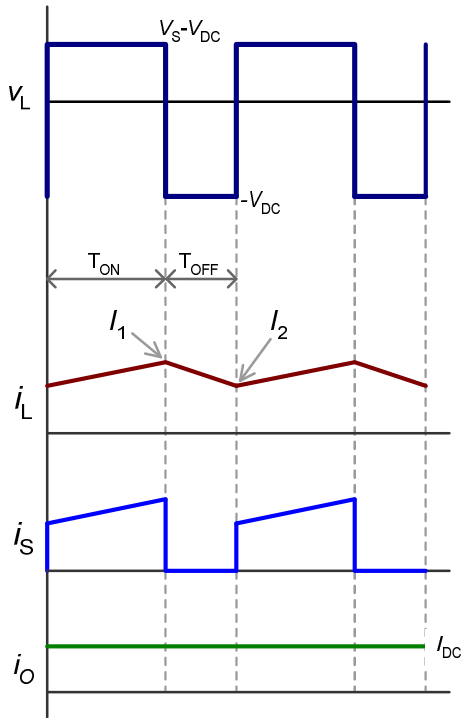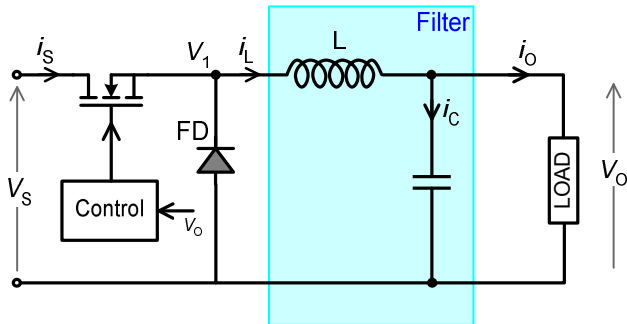

Voltage across inductor, $v_L = L \frac{di}{dt}$

During rise time of i_L

$$V_S - V_{DC} = L \frac{I_2 - I_1}{T_{ON}} = L \frac{\Delta I}{T_{ON}}$$

$$T_{ON} = \frac{L \Delta I}{V_S - V_{DC}}$$

During fall time of i_L

$$-V_{DC} = L \frac{I_1 - I_2}{T_{OFF}} = L \frac{\Delta I}{T_{OFF}}$$

$$T_{OFF} = \frac{L \Delta I}{V_{DC}}$$

Equating ΔI from the two expressions

$$\Delta I = \frac{(V_S - V_{DC}) T_{ON}}{L} = \frac{V_{DC} T_{OFF}}{L}$$

$$T = T_{ON} + T_{OFF}$$

If α is duty cycle

$$T_{ON} = \alpha T \quad T_{OFF} = (1 - \alpha) T$$

$$\alpha = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

$$V_{DC} = \alpha V_S$$

$$\alpha = \frac{V_{DC}}{V_S}$$

$$T = \frac{1}{f} = T_{ON} + T_{OFF}$$

$$= \frac{L \Delta I}{V_S - V_{DC}} + \frac{L \Delta I}{V_{DC}} = \frac{V_{DC} L \Delta I + (V_S - V_{DC}) L \Delta I}{V_{DC} (V_S - V_{DC})} = \frac{V_S L \Delta I}{V_{DC} (V_S - V_{DC})}$$

$T_{ON} = \frac{L \Delta I}{V_S - V_{DC}}$
 $T_{OFF} = \frac{L \Delta I}{V_{DC}}$

ie. $\frac{1}{f} = \frac{V_S L \Delta I}{V_{DC} (V_S - V_{DC})}$

$$\Delta I = \frac{V_{DC} (V_S - V_{DC})}{V_S f L} = \frac{\alpha V_S (V_S - \alpha V_S)}{V_S f L} = \frac{V_S \alpha (1 - \alpha)}{f L}$$

$$\Delta I = \frac{V_S \alpha (1 - \alpha)}{f L}$$


Applying KCL

$$i_L = i_C + i_O$$

If load ripple current is assumed to be zero

$$\Delta i_L = \Delta i_C$$

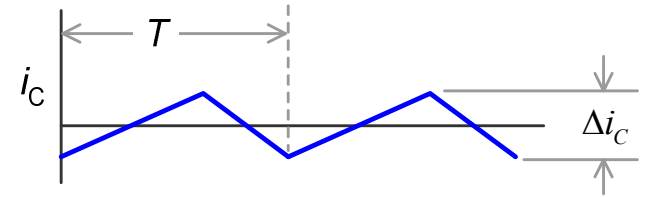Average capacitor current for a duration $\frac{T}{2}$, $I_C = \frac{\Delta I}{4}$



Peak-to-peak ripple voltage of capacitor, $\Delta v_C = \frac{1}{C} \int_0^{T/2} \frac{\Delta I}{4} dt = \frac{\Delta I T}{8C} = \frac{\Delta I}{8 C f}$

Substituting the value of ΔI

$$\Delta v_C = \frac{V_s \alpha (1 - \alpha)}{8 f^2 LC}$$

$$\Delta I = \frac{V_s \alpha (1 - \alpha)}{f L}$$

Example

A buck regulator has an input voltage of 120V, and the average output voltage is 70V. Average load current is 25A and the switching frequency of 25 kHz. The peak to peak ripple current in inductor is limited to 1A and the peak-to-peak ripple voltage at the output is 2V. Find the value of inductor and capacitor.

Applicable equations:

$$\Delta I = \frac{V_s \alpha (1 - \alpha)}{f L}$$

$$\Delta v_C = \frac{V_s \alpha (1 - \alpha)}{8 f^2 LC}$$

Solution

$$\text{Duty cycle, } \alpha = \frac{V_{DC}}{V_s} = \frac{70}{120} = 0.5833$$

$$\Delta I = \frac{V_s \alpha (1 - \alpha)}{f L}$$

$$1.0 = \frac{120 \times 0.5833 (1 - 0.5833)}{25 \times 10^3 \times L}$$

$$L = 1.17 \text{ mH}$$

$$\Delta v_c = \frac{V_s \alpha (1 - \alpha)}{8 f^2 LC}$$


$$2.0 = \frac{120 \times 0.5833 (1 - 0.5833)}{8 (25 \times 10^3)^2 \times 1.17 \times 10^{-3} \times C}$$

$$C = 2.49 \text{ } \mu\text{F}$$

Typical MOSFETS

IRFP250N


HEXFET® Power MOSFET

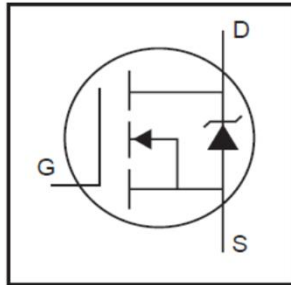

$V_{DSS} = 200V$
$R_{DS(on)} = 0.075\Omega$
$I_D = 30A$


utilize advanced processing over silicon area. This benefit, optimized device design that provides the designer with an wide variety of applications.

Industrial applications where efficiency is critical. The TO-247 is similar to its isolated mounting hole.

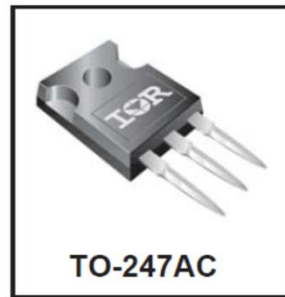


VMO 650-01F

V_{DSS}	$= 100 V$
I_{D25}	$= 690 A$
$R_{DS(on)}$	$= 1.8 m\Omega$

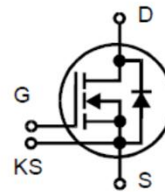

RU E 72873

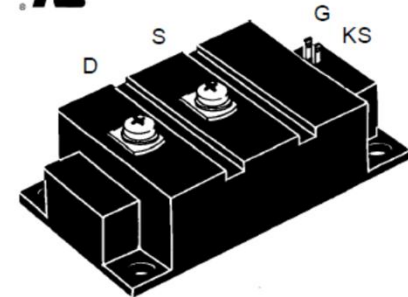

D = Drain S = Source
KS = Kelvin Source G = Gate

Maximum Ratings

100	V
100	V
±20	V
±30	V


Typical IGBTs

HGTG30N120D2

30A, 1200V N-Channel IGBT

Package

JEDEC STYLE TO-247

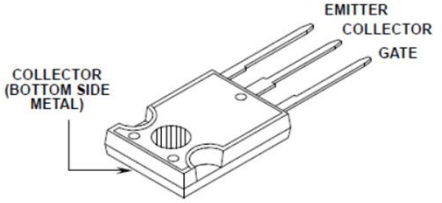


EMITTER
COLLECTOR
GATE

COLLECTOR
(BOTTOM SIDE
METAL)

Package switching
Ts and bipolar
ince of a MOS-
polar transistor.
nly moderately

Terminal Diagram

N-CHANNEL ENHANCEMENT MODE

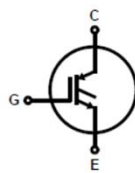

C
G
E

BRAND
120D2

MITSUBISHI IGBT MODULES
CM50DY-28H
MEDIUM POWER SWITCHING USE
INSULATED TYPE

